



**AVIT**  
AARUPADAI VEEDU INSTITUTE OF TECHNOLOGY



VINAYAKA MISSION'S  
RESEARCH FOUNDATION  
(Deemed to be University under section 3 of the UGC Act 1956)



**DEPARTMENT OF ELECTRONICS AND COMMUNICATION ENGINEERING**

# **DIGITAL LOGIC CIRCUITS & DESIGN LAB**

**Program/ Branch** : B. E., /ECE  
**Year / Semester** : II/ III  
**Academic Year** : 2021 – 2022 (Odd Semester)  
**Regulation** : R 2017

**HOD / ECE**

17ECCC82	DIGITAL LOGIC CIRCUITS & DESIGN LAB					Category	L	T	P	Credit					
						CC	0	0	4	2					
<b>PREAMBLE</b> To provide experience & explore designs in analyzing and testing of digital logic circuits like combinational and sequential circuits using lab instruments as well as simulation software. <b>Prerequisite</b> : Basic Electrical and Electronics Engineering															
<b>PREREQUISITE</b> 17EEES03 - Basics of Electrical and Electronics Engineering															
<b>COURSE OBJECTIVES</b>															
1	To impart the knowledge in analysis and design of various combinational logic circuits.														
2	To learn about design and analysis of sequential circuits using flip flops.														
3	To Expose students about design and simulation of logic circuits using HDL.														
<b>COURSE OUTCOMES</b>															
On the successful completion of the course, students will be able to															
CO1. Construct various logic circuits.									Apply						
CO2. Demonstrate the various combinational logic circuits by using discrete components									Apply						
CO3. Analyze different sequential logic circuits by using discrete components.									Analyze						
CO4. Test the various digital logic circuits by using simulation software.									Evaluate						
CO5. Measure and record the experimental data for various digital circuits.									Evaluate						
<b>MAPPING WITH PROGRAMME OUTCOMES AND PROGRAMME SPECIFIC OUTCOMES</b>															
COs	PO1	PO2	PO3	PO4	PO5	PO6	PO7	PO8	PO9	PO10	PO11	PO12	PSO1	PSO2	PSO3
CO1	S	-	-	-	M	-	-	-	M	-	-	L	S	-	-
CO2	S	-	-	-	S	-	-	-	M	-	-	L	S	M	-
CO3	S	M	M	M	M	-	-	-	M	-	-	L	S	M	-
CO4	S	M	-	-	M	-	-	-	M	-	-	L	S	S	M
CO5	S	M	-	-	M	-	-	-	M	-	-	L	S	M	-
S- Strong; M-Medium; L-Low															

### List of Experiments

#### Hardware Experiments

- Design and implementation of Adders using logic gates.
- Design and implementation of Sub tractors using logic gates.
- Design and implementation of BCD to Excess -3 code converter using logic gates
- Design and implementation of Binary to Gray code converter using logic gates
- Design and implementation of 4 bit BCD adder using IC 7483
- Design and implementation of 2 Bit Magnitude comparator using logic gates
- Design and implementation of Multiplexer and De-Multiplexer using logic gates
- Design and implementation of encoder and decoder using logic gates
- Design and implementation of 3 bit synchronous up/down counter.
- Implementation of SISO, SIPO, and PISO shift registers using flip flops.

#### Software Experiments using HDL

- Design and Simulation of Full adder circuit using Gate level modelling
- Design and Simulation of 2X2 multiplier circuit using structural level modeling.
- Design and Simulation of 8 to 1 Multiplexer circuit using behavioural level modeling.

### COURSE DESIGNERS

S.No.	Name of the Faculty	Designation	Department	Mail ID
1	Mr.B.Rajasekaran	Associate Professor	ECE	rajasekaran@vmkvec.edu.in
2	Mrs.S.Valarmathy	Associate Professor	ECE	valarmathy@vmkvec.edu.in
3	Ms.R.Mohana Priya	Assistant Professor (Gr-II)	ECE	mohanapriya@avit.ac.in




HOD / ECE

<b>EXPT. NO</b>	<b>NAME OF THE EXPERIMENT</b>	<b>PAGE NO</b>
	Study of Logic Gates	2
1.	Design and implementation of Adder and Subtractor using Logic gates	8
2.	Design and implementation of code converters using logic gates (i) BCD to excess-3 code and vice versa. (ii) Binary to gray and vice versa	14
3.	Design and implementation of 4 bit binary Adder/ Subtractor and BCD Adder using IC 7483	24
4.	Design and implementation of 2-bit Magnitude Comparator using logic gates and 8-bit Magnitude Comparator using IC 7485	30
5.	Design and implementation of Multiplexer and Demultiplexer using logic gates	36
6.	Design and implementation of encoder and decoder using logic gates	40
7.	Design and implementation of 16-bit odd/ even parity checker generator using IC74180	44
8.	Construction and verification of 4-bit ripple counter and Mod-10/ Mod-12 Ripple counters	48
9.	Design and implementation of 3-bit synchronous up/down counter	56
10.	Implementation of SISO, SIPO, PISO and PIPO shift registers using Flip-flops	60
11.	Design of experiments 1, 5, 8 and 10 using Verilog Hardware Description Language	68

**HOD / ECE**

**AND gate:**


**SYMBOL**

 

**TRUTH TABLE**


A	B	F= A.B
0	0	0
0	1	0
1	0	0
1	1	1

**PIN DIAGRAM**

 

**3-Input AND gate:**


**SYMBOL**

 

**TRUTH TABLE**

A	B	C	F= A.B.C
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	1

**PIN DIAGRAM**

 

*Handwritten signature*

# STUDY OF LOGIC GATES

## AIM:

To study about logic gates and verify their truth tables.

## APPARATUS REQUIRED:

SL.NO	COMPONENTS	SPECIFICATION	QUANTITY
1.	2- I/P AND gate	IC 7408	1
2.	3-I/P AND gate	IC7411	1
3.	OR gate	IC 7432	1
4.	NOT gate	IC 7404	1
5.	2- I/P NAND gate	IC7400	1
6.	3-I/P NAND gate	IC7410	1
7.	NOR gate	IC7402	1
8.	EX-OR gate	IC7486	1
9.	IC Trainer Kit	-	1
10.	Patch cords	-	Few

## THOERY:

Logic gates are the basic elements that make up a digital system. The gate is a digital circuit with one or more inputs, but only one output. By connecting the different gates in different ways, we can build circuits that perform arithmetic and other functions.

The operation of a logic gate can be easily understood with the help of “truth table”. A truth table is a table that shows all the input-output possibilities of a logic circuit ie., the truth table indicates the outputs for different possibilities of the inputs.

The types of gates available are the AND, OR, NOT, NAND, NOR, exclusive-OR and the exclusive-NOR. Except for the exclusive-NOR gate they are available in monolithic integrated form.

### **AND gate:**

The AND gates has two or more inputs. It performs a logical multiplication. The output is HIGH (1), when both the inputs are 1; otherwise the output from the gate is LOW (0). The output from the AND gate is written as **A.B**.



**HOD / ECE**

**OR gate:**


**SYMBOL**



**TRUTH TABLE**


A	B	F= A+B
0	0	0
0	1	1
1	0	1
1	1	1

**PIN DIAGRAM**

 

**NOT gate:**


**SYMBOL**

 

**TRUTH TABLE**

A	F= Ā
0	1
1	0

**PIN DIAGRAM**

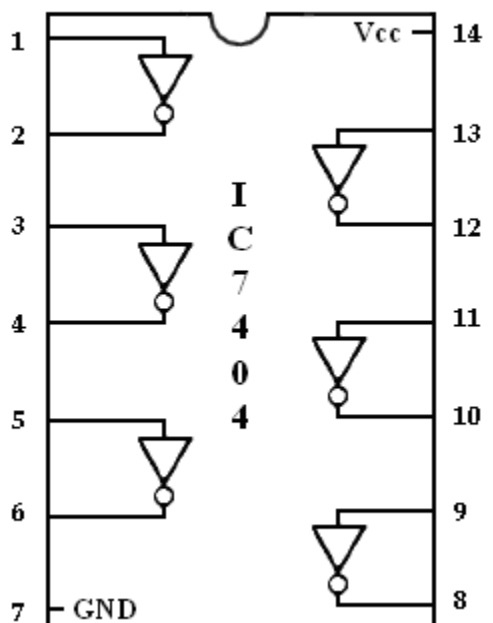

*Handwritten signature*

**OR gate:**

The OR gate has two or more inputs. It performs a logical addition. The output is HIGH (1), if any of the inputs are 1; the output is LOW (0) if and only if all the inputs are 0. The output from the OR gate is written as  $A+B$ .

**NOT gate:**

The NOT gate has only one input. It performs a basic logic function called inversion. The output is HIGH (1), when the input is 0; the output is LOW (0) when the input is 1. The output from the NOT gate is written as  $A'$ .

**NAND gate:**

The NAND gate is a contraction of AND-NOT. It has two or more inputs. The output is HIGH (1), when any of the inputs are 0; the output is LOW (0), if and only if all the inputs are 1. The output from the AND gate is written as  $(A \cdot B)'$ . It is a universal gate.

**NOR gate:**

The NOR gate is a contraction of OR-NOT. It has two or more inputs. The output is HIGH (1), when all inputs are 0; the output is LOW (0), when any of the inputs are 1. The output from the AND gate is written as  $(A+B)'$ . It is a universal gate.

**EX-OR gate:**

The EX-OR gate has two or more inputs. The output is HIGH (1), when odd number of inputs is 1. The output from the AND gate is written as  $(A \oplus B)$ .


**PROCEDURE:**

1. Connections are given as per the logic diagram.
2. Logic inputs are given as per the truth table.
3. Observe the logic output and verify with the truth table.

**HOD / ECE**

**2-Input NAND gate:**


**SYMBOL**

 

**TRUTH TABLE**


A	B	F = $\overline{A \cdot B}$
0	0	1
0	1	1
1	0	1
1	1	0

**PIN DIAGRAM**

 

**3-Input NAND gate:**


**SYMBOL**

 

**TRUTH TABLE**

A	B	C	F = $\overline{A \cdot B \cdot C}$
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	0

**PIN DIAGRAM**

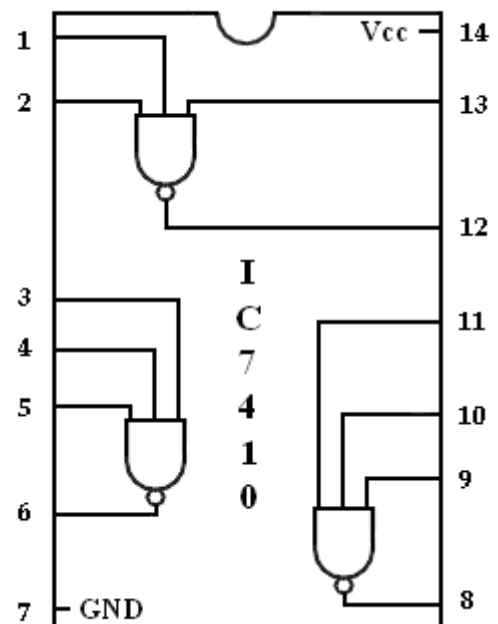


*Handwritten signature*



**NOR gate:**


**SYMBOL**

 

**TRUTH TABLE**


A	B	$F = \overline{A+B}$
0	0	1
0	1	0
1	0	0
1	1	0

**PIN DIAGRAM**

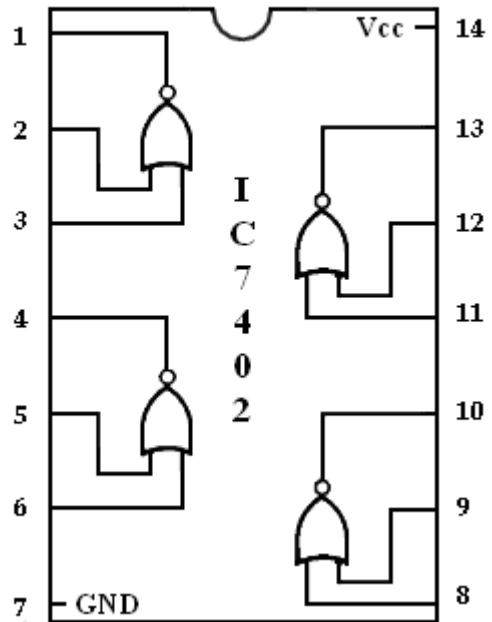

**EX-OR gate:**


**SYMBOL**

 

**TRUTH TABLE**

A	B	$F = A \oplus B$
0	0	0
0	1	1
1	0	1
1	1	0

**PIN DIAGRAM**

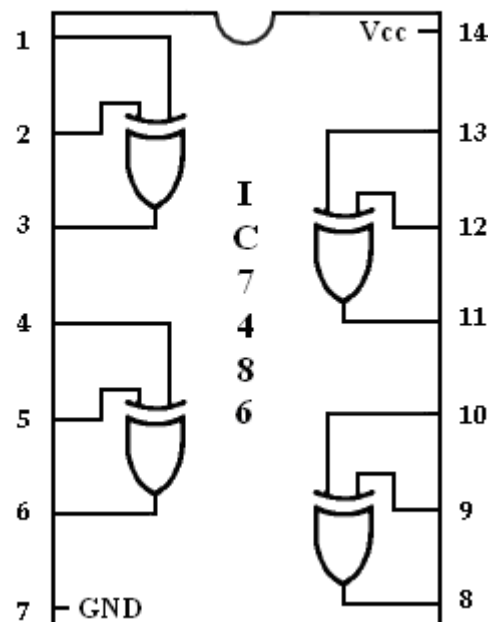

**RESULT:**

Thus the logic gates are studied and their truth tables are verified.

*Handwritten signature*


**HOD / ECE**

## HALF ADDER:


### TRUTH TABLE:

Inputs		Outputs	
A	B	Carry (C)	Sum (S)
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

### K- MAP SIMPLIFICATION:

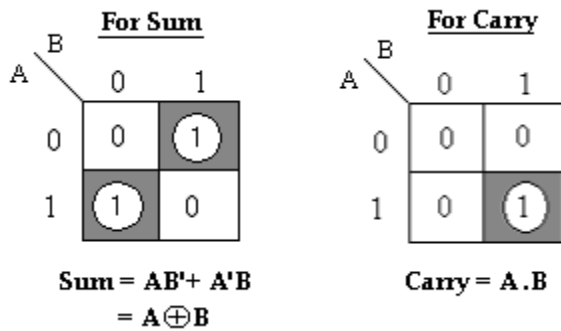

### LOGIC DIAGRAM:

 

## FULL ADDER:

### TRUTH TABLE:

Inputs			Outputs	
A	B	C <sub>in</sub>	Sum (S)	Carry (C <sub>out</sub> )
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

*Handwritten signature*

EX.NO: 1

DATE :

## DESIGN OF ADDER & SUBTRACTOR

### AIM:

To design and construct a half adder, full adder, half subtractor and full subtractor circuits and verify their truth table using logic gates.

### APPARATUS REQUIRED:

SL.NO	COMPONENTS	SPECIFICATION	QUANTITY
1.	IC Trainer kit	-	1
2.	EX-OR gate	IC 7486	1
3.	NOT gate	IC 7404	1
4.	OR gate	IC 7432	1
5.	AND gate	IC7408	1
6.	Patch cords	-	Few

### THEORY:

#### **Half Adder:**

A half-adder is a combinational circuit that can be used to add two binary bits. It has two inputs that represent the two bits to be added and two outputs, with one producing the SUM output and the other producing the CARRY. The Sum can be applied using EX-OR gate, carry output can be applied using an AND gate.

#### **Full Adder:**

A full adder is a combinational circuit that forms the arithmetic sum of three input bits. It consists of 3 inputs and 2 outputs. Two of the input variables, represent the significant bits to be added. The third input represents the carry from previous lower significant position.

The logic diagram of the full adder can also be implemented with two half-adders and one OR gate. The S output from the second half adder is the exclusive-OR of  $C_{in}$  and the output of the first half-adder



HOD / ECE

**K-MAP SIMPLIFICATION:**

**For Sum**

A \ BC <sub>in</sub>	00	01	11	10
0	0	1	0	1
1	1	0	1	0

**Sum, S** =  $A'B'C_{in} + A'BC'_{in} + AB'C'_{in} + ABC_{in}$   
 =  $C_{in} \oplus (A \oplus B)$


**For Carry**

A \ BC <sub>in</sub>	00	01	11	10
0	0	0	1	0
1	0	1	1	1


**Carry, C<sub>out</sub>** =  $AB + AC_{in} + BC_{in}$

**LOGIC DIAGRAM:**

**Full Adder:**

 

**Full Adder using Two Half Adders:**

 

*Handwritten signature*

**Half Subtractor:**

A half-subtractor is a combinational circuit that can be used to subtract one binary digit from another to produce a DIFFERENCE output and a BORROW output. The BORROW output here specifies whether a '1' has been borrowed to perform the subtraction. The difference can be applied using EX-OR gate, borrow output can be applied using an AND gate and an inverter.

**Full Subtractor:**

A full subtractor performs subtraction operation on two bits, a minuend and a subtrahend, and also takes into consideration whether a '1' has already been borrowed by the previous adjacent lower minuend bit or not.

As a result, there are three bits to be handled at the input of a full subtractor, namely the two bits to be subtracted and a borrow bit designated as  $B_{in}$ . There are two outputs, namely the DIFFERENCE output  $D$  and the BORROW output  $B_o$ . The BORROW output bit tells whether the minuend bit needs to borrow a '1' from the next possible higher minuend bit.

**PROCEDURE:**


1. Connections are given as per the logic diagram.
2. Logic inputs are given as per the truth table.
3. Observe the logic output and verify with their truth tables.

**HALF SUBTRACTOR:****HOD / ECE**


**TRUTH TABLE:**

Input		Output	
A	B	Difference (D)	Borrow (B <sub>out</sub> )
0	0	0	0
0	1	1	1
1	0	1	0
1	1	0	0

**K- MAP SIMPLIFICATION:**

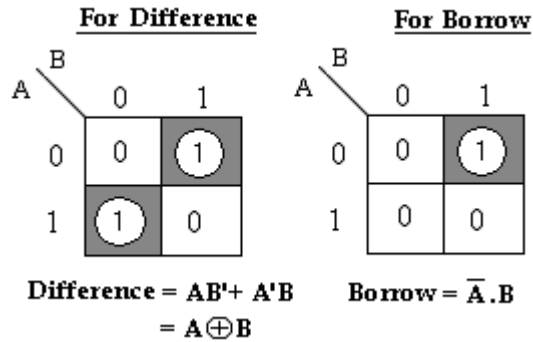

**LOGIC DIAGRAM:**

 

**FULL SUBTRACTOR:**

**TRUTH TABLE:**

Inputs			Outputs	
A	B	B <sub>in</sub>	Difference(D)	Borrow(B <sub>out</sub> )
0	0	0	0	0
0	0	1	1	1
0	1	0	1	1
0	1	1	0	1
1	0	0	1	0
1	0	1	0	0
1	1	0	0	0
1	1	1	1	1

**K- MAP SIMPLIFICATION:**

*Handwritten signature*

**For Difference**

	$B B_{in}$	00	01	11	10
A	0	0	1	0	1
	1	1	0	1	0

**For Borrow**


	$B B_{in}$	00	01	11	10
A	0	0	1	1	1
	1	0	0	1	0

**Difference,  $D = A'B'B_{in} + A'BB'_{in} + AB'B'_{in} + ABB_{in}$**   
 $= B_{in} \oplus (A \oplus B)$


**Borrow,  $B_{out} = A'B + A'B_{in} + BB_{in}$**

**LOGIC DIAGRAM:**

**Full Subtractor:**

 

 **Full Subtractor with Two Half Subtractors:**



**RESULT:**

Thus half adder, full adder, half subtractor and full subtractor circuits was designed using logic gates and their truth tables were verified.

**BINARY TO GRAY CODE CONVERTER:**

*Handwritten signature*

**TRUTH TABLE:**

Binary code				Gray code			
B <sub>3</sub>	B <sub>2</sub>	B <sub>1</sub>	B <sub>0</sub>	G <sub>3</sub>	G <sub>2</sub>	G <sub>1</sub>	G <sub>0</sub>
0	0	0	0	0	0	0	0
0	0	0	1	0	0	0	1
0	0	1	0	0	0	1	1
0	0	1	1	0	0	1	0
0	1	0	0	0	1	1	0
0	1	0	1	0	1	1	1
0	1	1	0	0	1	0	1
0	1	1	1	0	1	0	0
1	0	0	0	1	1	0	0
1	0	0	1	1	1	0	1
1	0	1	0	1	1	1	1
1	0	1	1	1	1	1	0
1	1	0	0	1	0	1	0
1	1	0	1	1	0	1	1
1	1	1	0	1	0	0	1
1	1	1	1	1	0	0	0

**K- Map Simplification:**

For G<sub>3</sub>

B <sub>3</sub> B <sub>2</sub> \ B <sub>1</sub> B <sub>0</sub>	00	01	11	10
00	0	0	0	0
01	0	0	0	0
11	1	1	1	1
10	1	1	1	1

$$G_3 = B_3$$

For G<sub>2</sub>

B <sub>3</sub> B <sub>2</sub> \ B <sub>1</sub> B <sub>0</sub>	00	01	11	10
00	0	0	0	0
01	1	1	1	1
11	0	0	0	0
10	1	1	1	1

$$G_2 = B_3'B_2 + B_3B_2'$$

$$= B_3 \oplus B_2$$

For G<sub>1</sub>

B <sub>3</sub> B <sub>2</sub> \ B <sub>1</sub> B <sub>0</sub>	00	01	11	10
00	0	0	1	1
01	1	1	0	0
11	1	1	0	0
10	0	0	1	1

$$G_1 = B_2'B_1 + B_2B_1'$$

$$= B_2 \oplus B_1$$

For G<sub>0</sub>

B <sub>3</sub> B <sub>2</sub> \ B <sub>1</sub> B <sub>0</sub>	00	01	11	10
00	0	1	0	1
01	0	1	0	1
11	0	1	0	1
10	0	1	0	1

$$G_0 = B_1'B_0 + B_1B_0'$$

$$= B_1 \oplus B_0$$

*Handwritten signature*



**EX.NO: 2**

**DATE :**

## **DESIGN AND IMPLEMENTATION OF CODE CONVERTERS**

### **AIM:**

To design and implement 4-bit

1. Binary to Gray code Converter
2. Gray to Binary code Converter
3. BCD to Excess-3 code Converter
4. Excess-3 code to BCD Converter

### **APPARATUS REQUIRED:**

<b>SL.NO</b>	<b>COMPONENTS</b>	<b>SPECIFICATION</b>	<b>QUANTITY</b>
1.	IC Trainer kit	-	1
2.	EX-OR gate	IC7486	1
3.	NOT gate	IC7404	1
4.	OR gate	IC7432	1
5.	2-Input AND gate	IC7408	1
6.	3-Input AND gate	IC7411	1
7.	Patch cords	-	As Required

### **THEORY:**


An availability of large variety of codes for the same discrete elements of information results in the use of different codes by different systems. A conversion circuit must be inserted between the two systems if each uses different codes for the same information. Thus, code converter is a circuit that makes the two systems compatible even though each uses different binary code.

The input variable are designed as  $B_3, B_2, B_1, B_0$  and the output variables are designed as  $G_3, G_2, G_1, G_0$ . From the truth table, combinational circuit is designed. The Boolean functions are obtained from K-Map for each output variable.



**HOD / ECE**

**Logic Diagram:**

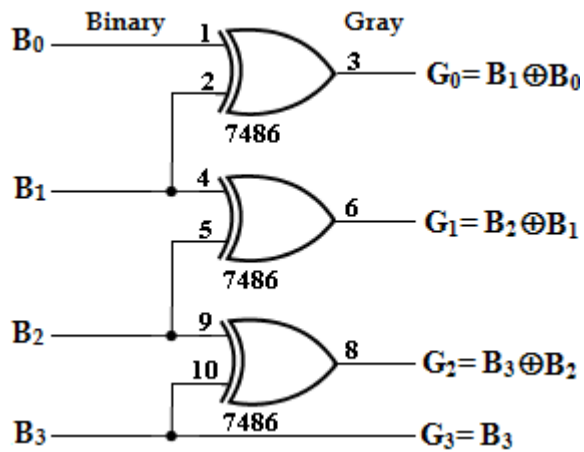

**GRAY TO BINARY CODE CONVERTER:**

**TRUTH TABLE:**

Gray code				Binary code			
$G_3$	$G_2$	$G_1$	$G_0$	$B_3$	$B_2$	$B_1$	$B_0$
0	0	0	0	0	0	0	0
0	0	0	1	0	0	0	1
0	0	1	0	0	0	1	1
0	0	1	1	0	0	1	0
0	1	0	0	0	1	1	1
0	1	0	1	0	1	1	0
0	1	1	0	0	1	0	0
0	1	1	1	0	1	0	1
1	0	0	0	1	1	1	1
1	0	0	1	1	1	1	0
1	0	1	0	1	1	0	0
1	0	1	1	1	1	0	1
1	1	0	0	1	0	0	0
1	1	0	1	1	0	0	1
1	1	1	0	1	0	1	1
1	1	1	1	1	0	1	0

*Handwritten signature*

To convert from binary code to Excess-3 code, the input lines must supply the bit combination of elements as specified by code and the output lines generate the corresponding bit combination of code. Each one of the four maps represents one of the four outputs of the circuit as a function of the four input variables.

A two-level logic diagram may be obtained directly from the Boolean expressions derived by the maps. These are various other possibilities for a logic diagram that implements this circuit.

**PROCEDURE:**

1. Connections are given as per the logic diagram.
2. Logic inputs are given as per the truth table.
3. Observe the logic output and verify with the truth tables.



**HOD / ECE**

**K-Map Simplification:**

For B<sub>3</sub>

	$G_1 G_0$	00	01	11	10
$G_3 G_2$	00	0	0	0	0
	01	0	0	0	0
	11	1	1	1	1
	10	1	1	1	1

$B_3 = G_3$

For B<sub>2</sub>

	$G_1 G_0$	00	01	11	10
$G_3 G_2$	00	0	0	0	0
	01	1	1	1	1
	11	0	0	0	0
	10	1	1	1	1

$B_2 = G_3'G_2 + G_3G_2'$   
 $= G_3 \oplus G_2$

For B<sub>1</sub>

	$G_1 G_0$	00	01	11	10
$G_3 G_2$	00	0	0	1	1
	01	1	1	0	0
	11	0	0	1	1
	10	1	1	0	0


$B_1 = G_3 \oplus G_2 \oplus G_1$

For B<sub>0</sub>

	$G_1 G_0$	00	01	11	10
$G_3 G_2$	00	0	1	0	1
	01	1	0	1	0
	11	0	1	0	1
	10	1	0	1	0

$B_0 = (G_0 \oplus G_1) \oplus (G_2 \oplus G_3)$

**Logic Diagram:**

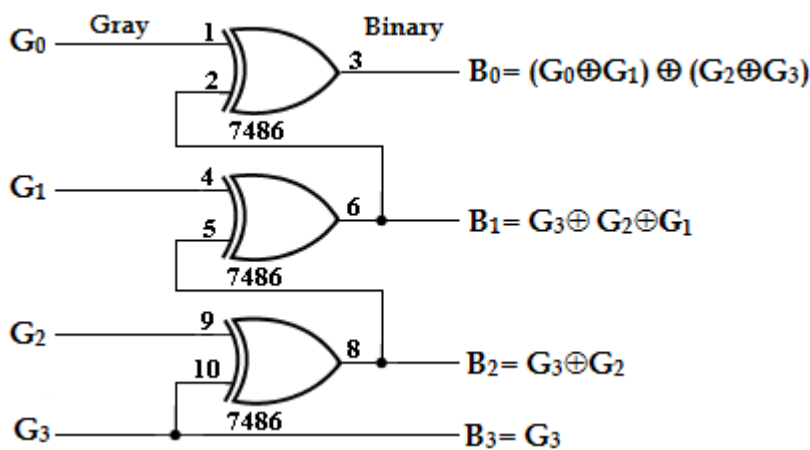

*Handwritten signature*

**BCD TO EXCESS-3 CODE:**

**Truth table:**

BCD code				Excess-3 code			
B <sub>3</sub>	B <sub>2</sub>	B <sub>1</sub>	B <sub>0</sub>	E <sub>3</sub>	E <sub>2</sub>	E <sub>1</sub>	E <sub>0</sub>
0	0	0	0	0	0	1	1
0	0	0	1	0	1	0	0
0	0	1	0	0	1	0	1
0	0	1	1	0	1	1	0
0	1	0	0	0	1	1	1
0	1	0	1	1	0	0	0
0	1	1	0	1	0	0	1
0	1	1	1	1	0	1	0
1	0	0	0	1	0	1	1
1	0	0	1	1	1	0	0

**K-Map Simplification:**

For E<sub>3</sub>

		B <sub>1</sub> B <sub>0</sub>			
		00	01	11	10
B <sub>3</sub> B <sub>2</sub>	00	0	0	0	0
	01	0	1	1	1
	11	x	x	x	x
	10	1	1	x	x

$$E_3 = B_3 + B_2 (B_0 + B_1)$$

For E<sub>2</sub>

		B <sub>1</sub> B <sub>0</sub>			
		00	01	11	10
B <sub>3</sub> B <sub>2</sub>	00	0	1	1	1
	01	1	0	0	0
	11	x	x	x	x
	10	0	1	x	x

$$E_2 = B_2 B_1' B_0' + B_2' (B_0 + B_1)$$

For E<sub>1</sub>

		B <sub>1</sub> B <sub>0</sub>			
		00	01	11	10
B <sub>3</sub> B <sub>2</sub>	00	1	0	1	0
	01	1	0	1	0
	11	x	x	x	x
	10	1	0	x	x

$$E_1 = B_1' B_0' + B_1 B_0$$

$$= B_1 \odot B_0$$

For E<sub>0</sub>


		B <sub>1</sub> B <sub>0</sub>			
		00	01	11	10
B <sub>3</sub> B <sub>2</sub>	00	1	0	0	1
	01	1	0	0	1
	11	x	x	x	x
	10	1	0	x	x

$$E_0 = B_0'$$

*Handwritten signature*

**Logic Diagram:**

**BCD Code**

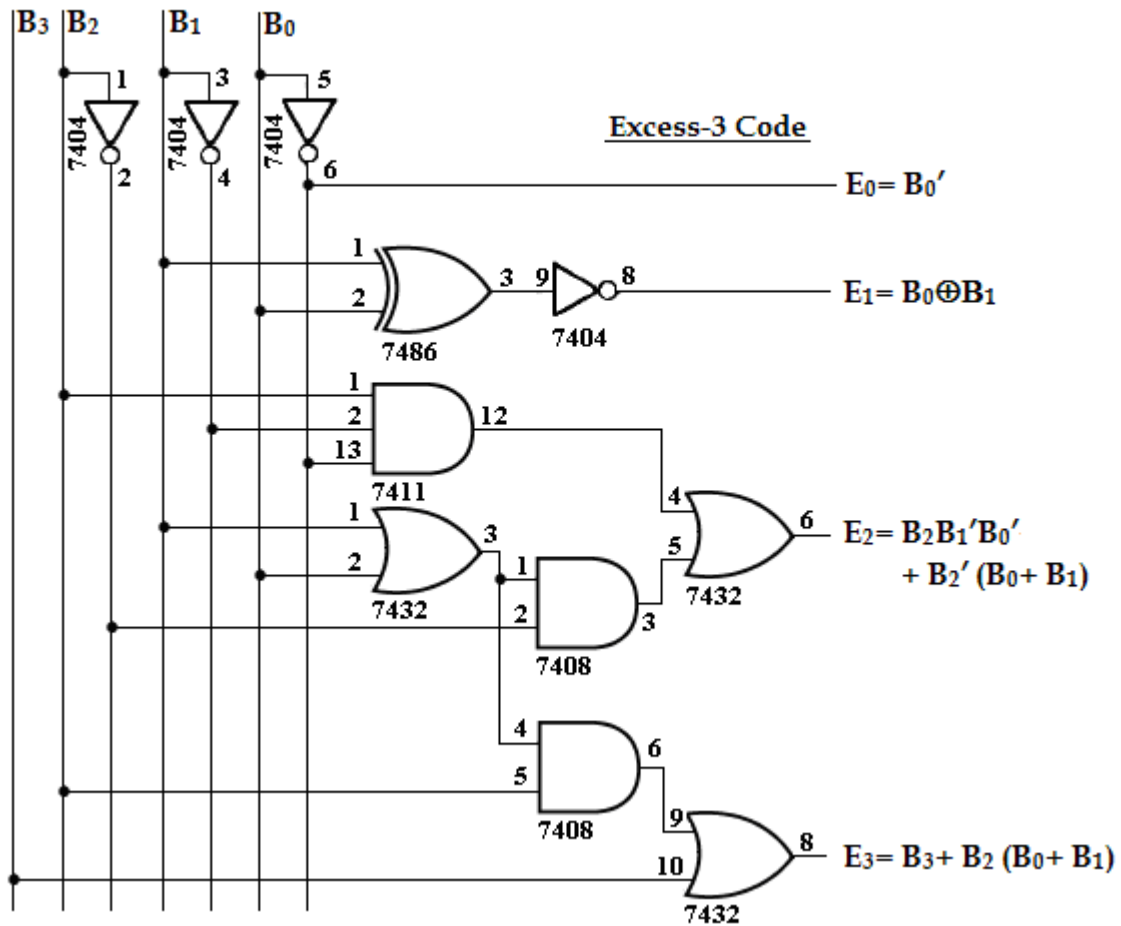

*Handwritten signature*

## EXCESS-3 TO BCD CONVERTER:

### Truth Table:

Excess-3 code				BCD code			
E <sub>3</sub>	E <sub>2</sub>	E <sub>1</sub>	E <sub>0</sub>	B <sub>3</sub>	B <sub>2</sub>	B <sub>1</sub>	B <sub>0</sub>
0	0	1	1	0	0	0	0
0	1	0	0	0	0	0	1
0	1	0	1	0	0	1	0
0	1	1	0	0	0	1	1
0	1	1	1	0	1	0	0
1	0	0	0	0	1	0	1
1	0	0	1	0	1	1	0
1	0	1	0	0	1	1	1
1	0	1	1	1	0	0	0
1	1	0	0	1	0	0	1

### K-Map Simplification:

For B<sub>3</sub>

		E <sub>1</sub> E <sub>0</sub>			
	E <sub>3</sub> E <sub>2</sub>	00	01	11	10
00		X	X	0	X
01		0	0	0	0
11		1	X	X	X
10		0	0	1	0

$$B_3 = E_3E_2 + E_3E_1E_0$$

For B<sub>2</sub>

		E <sub>1</sub> E <sub>0</sub>			
	E <sub>3</sub> E <sub>2</sub>	00	01	11	10
00		X	X	0	X
01		0	0	1	0
11		0	X	X	X
10		1	1	0	1

$$B_2 = E_2'E_1' + E_2E_1E_0 + E_2'E_0'$$

For B<sub>1</sub>

		E <sub>1</sub> E <sub>0</sub>			
	E <sub>3</sub> E <sub>2</sub>	00	01	11	10
00		X	X	0	X
01		0	1	0	1
11		0	X	X	X
10		0	1	0	1

$$B_1 = E_1'E_0 + E_1E_0'$$

$$= E_1 \oplus E_0$$

For B<sub>0</sub>


		E <sub>1</sub> E <sub>0</sub>			
	E <sub>3</sub> E <sub>2</sub>	00	01	11	10
00		X	X	0	X
01		1	0	0	1
11		1	X	X	X
10		1	0	0	1

$$B_0 = E_0'$$

*Handwritten signature*

## Logic Diagram:

### Excess-3 Code

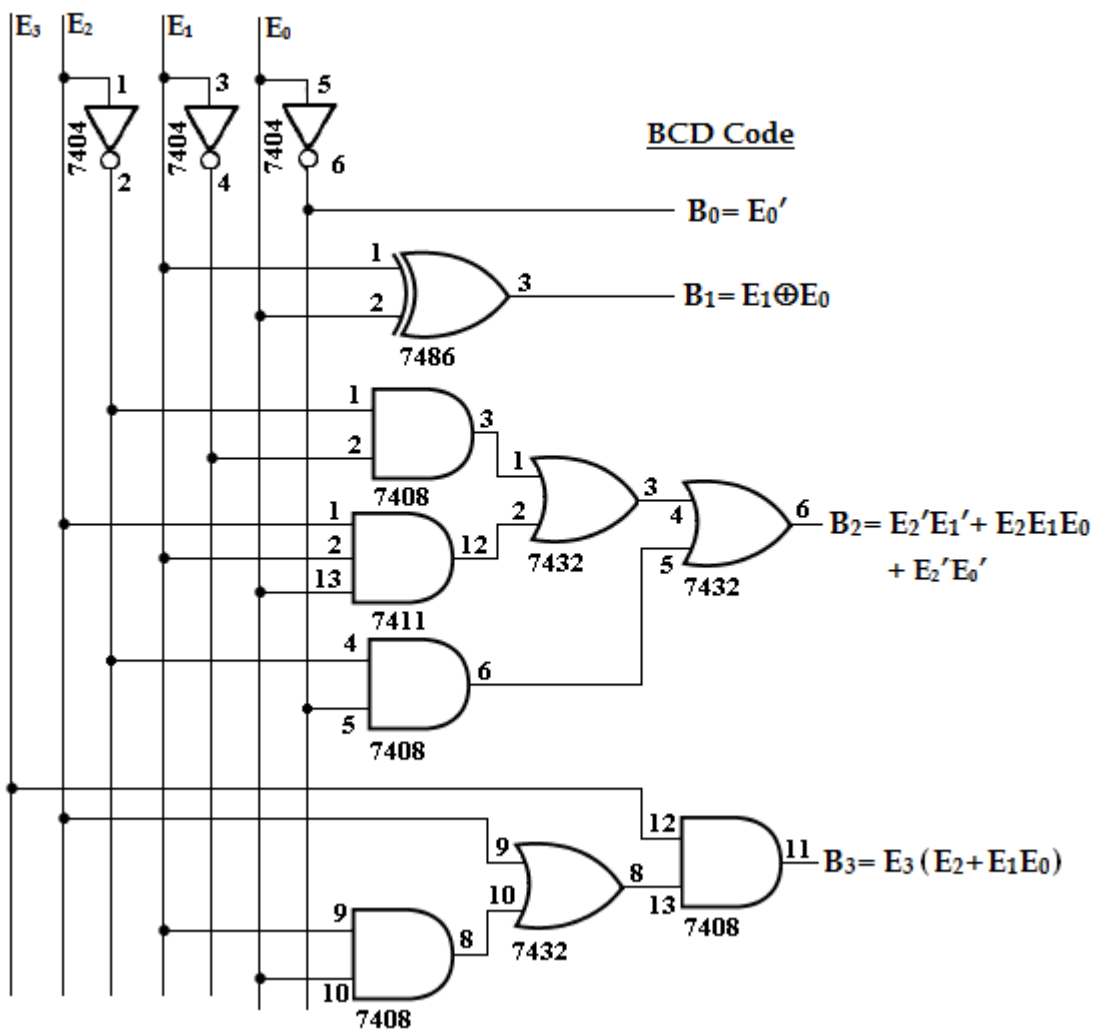

## RESULT:

Thus the 4-bit


1. Binary to Gray code Converter
2. Gray to Binary code Converter
3. BCD to Excess-3 code Converter
4. Excess-3 code to BCD Converter was designed and implemented.

HOD / ECE



## 4- BIT BINARY ADDER/ SUBTRACTOR:


### PIN DIAGRAM:

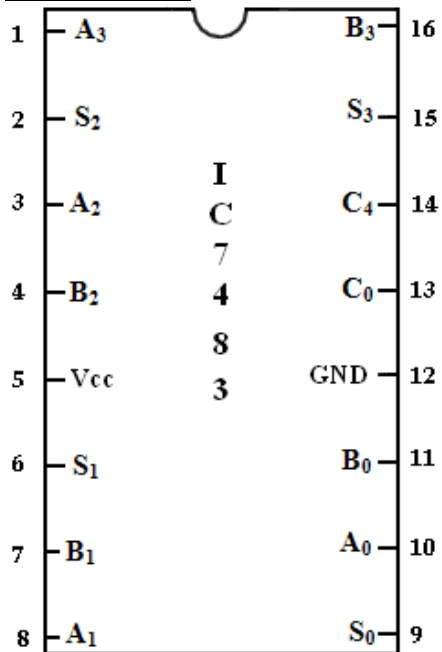

### LOGIC DIAGRAM:

*Handwritten signature*

HOD / ECE

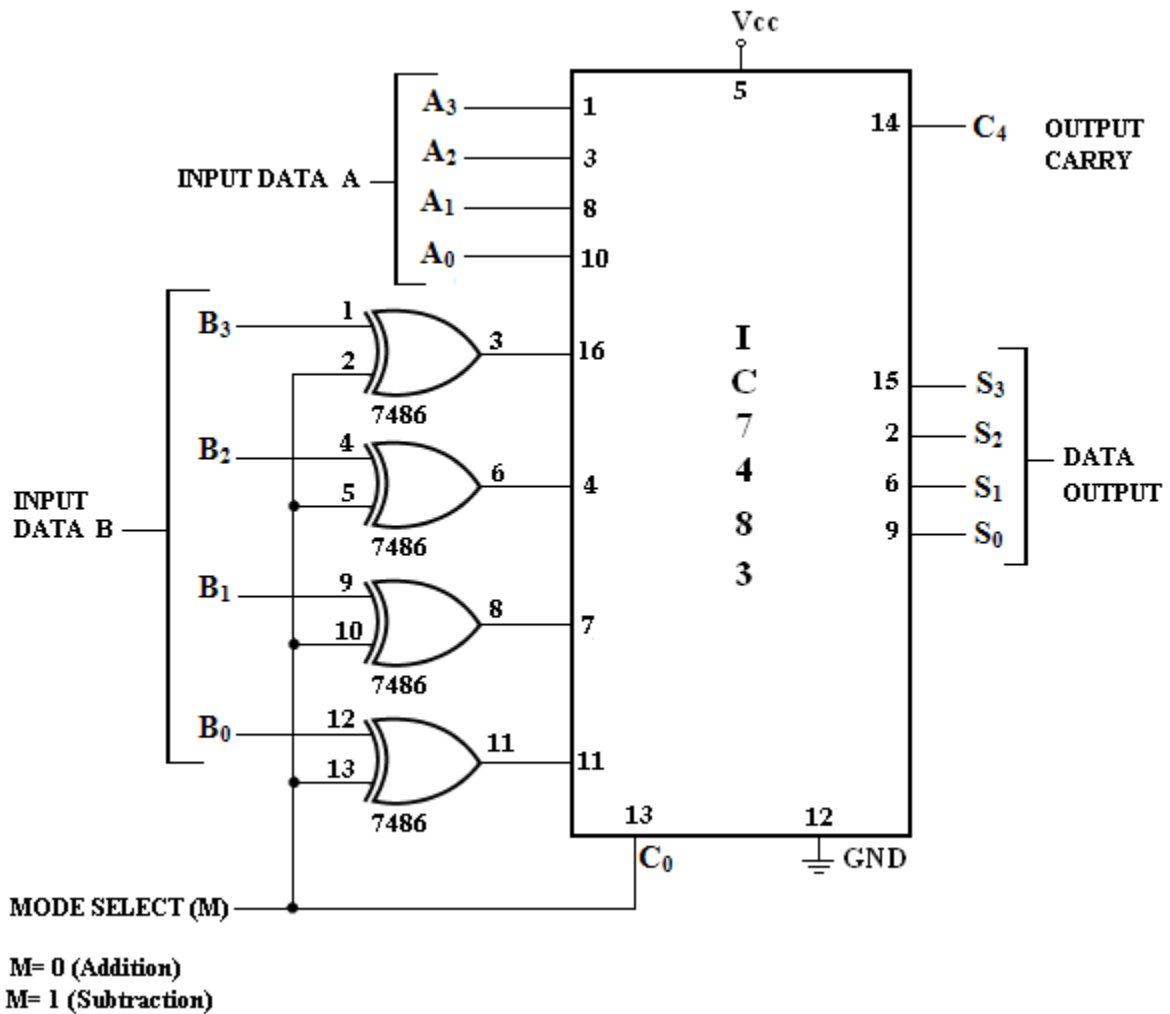

<b>EX.NO: 3</b> <b>DATE :</b>	<b>DESIGN OF 4-BIT ADDER/ SUBTRACTOR          &amp; BCD ADDER</b>
----------------------------------	---

**AIM:**

To Design and implement the 4-bit adder/ subtractor and BCD adder using IC 7483.

**APPARATUS REQUIRED:**

SL.NO	COMPONENT	SPECIFICATION	QUANTITY
-------	-----------	---------------	----------

*Handwritten signature*

**HOD / ECE**

1.	IC Trainer kit	-	1
2.	4-bit binary full adder	IC 7483	2
3.	EX-OR gate	IC 7486	1
4.	AND gate	IC 7408	1
5.	OR gate	IC 7432	1
6.	Patch cords	-	Few

### **THEORY:**

#### **4-Bit binary adder/ subtractor:**

The 4-bit binary adder/ subtractor circuit performs the operation of both addition and subtraction. It has two 4-bit inputs  $A_0, A_1, A_2, A_3$  and  $B_0, B_1, B_2, B_3$ . The mode input  $M$  controls the operation of the circuit. When  $M=0$ , the circuit is an adder and when  $M=1$ , the circuit becomes a Subtractor. Each exclusive-OR gate receives input  $M$  and one of the inputs of  $B$ .

When  $M=0$ , the operation is  $B \oplus 0 = B$ . The full adders receive the value of  $B$  and the input carry is 0, and the circuit performs the addition operation,  $A + B$ .

When  $M=1$ , the operation is  $B \oplus 1 = B'$  and  $C_0=1$ . The  $B$  inputs are all complemented and a 1 is added through the input carry. Thus the circuit performs the subtraction operation, i.e.,  $A + (2\text{'s complement of } B) = A - B$ .

### **TRUTH TABLE:**


Input data A				Input data B				Addition					Subtraction				
$A_3$	$A_2$	$A_1$	$A_0$	$B_3$	$B_2$	$B_1$	$B_0$	$C$	$S_3$	$S_2$	$S_1$	$S_0$	$B$	$D_3$	$D_2$	$D_1$	$D_0$
1	0	0	0	0	0	1	0	0	1	0	1	0	1	0	1	1	0
1	0	0	0	1	0	0	0	1	0	0	0	0	1	0	0	0	0
0	0	1	0	1	0	0	0	0	1	0	1	0	0	1	0	1	0
0	0	0	1	0	1	1	1	0	1	0	0	0	0	1	0	1	0
1	0	1	0	1	0	1	1	1	0	1	0	1	0	1	1	1	1
1	1	1	0	1	1	1	1	1	1	1	0	1	0	1	1	1	1
1	0	1	0	1	1	0	1	1	0	1	1	1	0	1	1	0	1

### **BCD ADDER:**



**HOD / ECE**

## LOGIC DIAGRAM:

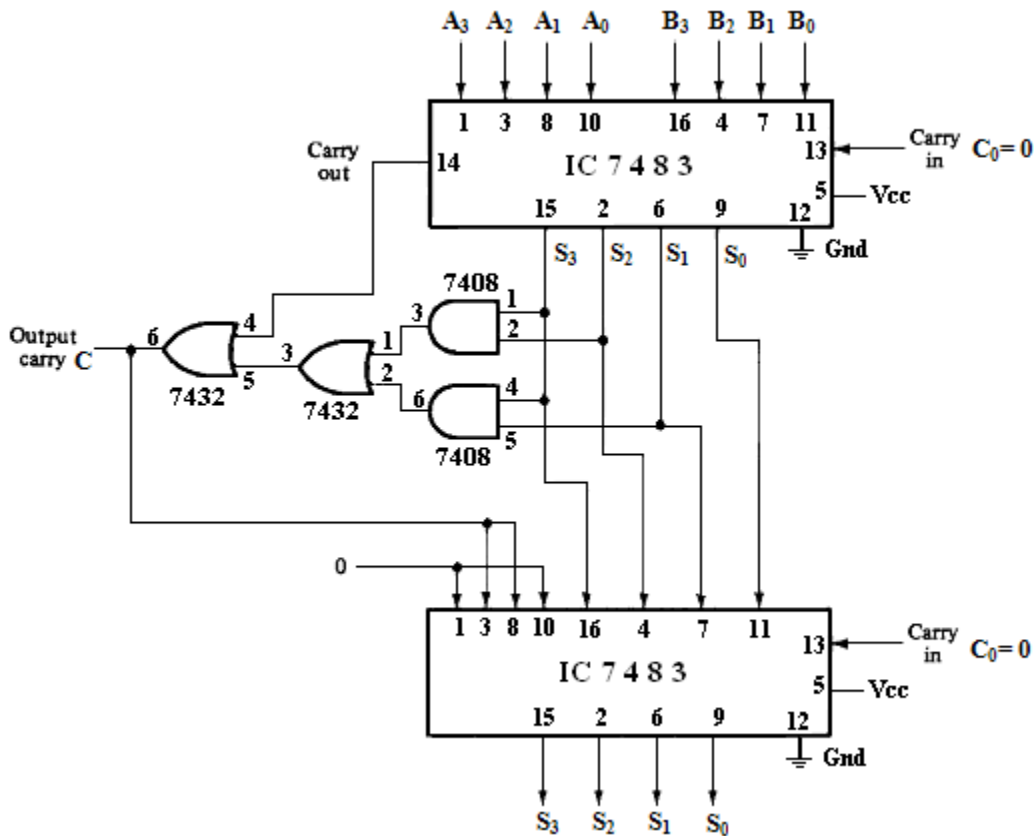

### 4- Bit BCD Adder:

The digital system handles the decimal number in the form of binary coded decimal numbers (BCD). A BCD adder is a circuit that adds two BCD bits and produces a sum digit also in BCD.

In examining the contents of the table, it is apparent that when the binary sum is equal to or less than  $(1001)_2$ , the corresponding BCD number is identical, and therefore no conversion is needed. When the binary sum is greater than 9  $(1001)_2$ , we obtain a non-valid BCD representation. The addition of binary 6  $(0110)_2$  to the binary sum converts it to the correct BCD representation and also produces an output carry as required.

The logic circuit to detect sum greater than 9 can be determined by simplifying the Boolean expression of the given truth table.

The two decimal digits, together with the input carry, are first added in the top 4-bit binary adder to provide the binary sum. When the output carry is equal to zero, nothing is added to the binary sum. When it is equal to one, binary  $(0110)_2$  is added to the binary sum through the bottom 4-bit adder. The output carry generated from the bottom adder can be ignored, since it supplies information already available at the output carry terminal. The output carry from one stage must be connected to the input carry of the next higher-order stage.

**PROCEDURE:**

1. Connections are given as per the logic diagram.
2. Logic inputs are given as per the truth table.
3. Observe the logic output and verify with the truth tables.

**Truth table:**



**HOD / ECE**

Inputs				Output
S <sub>3</sub>	S <sub>2</sub>	S <sub>1</sub>	S <sub>0</sub>	Y
0	0	0	0	0
0	0	0	1	0
0	0	1	0	0
0	0	1	1	0
0	1	0	0	0
0	1	0	1	0
0	1	1	0	0
0	1	1	1	0
1	0	0	0	0
1	0	0	1	0
1	0	1	0	1
1	0	1	1	1
1	1	0	0	1
1	1	0	1	1
1	1	1	0	1
1	1	1	1	1

S <sub>3</sub> S <sub>2</sub>		S <sub>1</sub> S <sub>0</sub>			
		00	01	11	10
00	01	0	0	0	0
01	11	0	0	0	0
11	10	1	1	1	1
10	0	0	1	1	

$$Y = S_3S_2 + S_3S_1$$

**RESULT:**

Thus the 4-bit adder/ subtractor and BCD adder using IC 7483 was designed and implemented.

**2-BIT MAGNITUDE COMPARATOR:**



**HOD / ECE**

**TRUTH TABLE:**

Inputs				Outputs		
A <sub>1</sub>	A <sub>0</sub>	B <sub>1</sub>	B <sub>0</sub>	A>B	A=B	A<B
0	0	0	0	0	1	0
0	0	0	1	0	0	1
0	0	1	0	0	0	1
0	0	1	1	0	0	1
0	1	0	0	1	0	0
0	1	0	1	0	1	0
0	1	1	0	0	0	1
0	1	1	1	0	0	1
1	0	0	0	1	0	0
1	0	0	1	1	0	0
1	0	1	0	0	1	0
1	0	1	1	0	0	1
1	1	0	0	1	0	0
1	1	0	1	1	0	0
1	1	1	0	1	0	0
1	1	1	1	0	1	0

**DESIGN:**

$$A = A_1A_0$$

$$B = B_1B_0$$

$$X_i = A_iB_i + A_i'B_i'$$

$$X_i = (A_i \oplus B_i)'$$

for  $i = 0, 1$

$$(A = B) = X_1 X_0$$

$$(A > B) = A_1B_1' + X_1A_0B_0'$$

$$(A < B) = A_1'B_1 + X_1A_0'B_0$$



**HOD / ECE**

<b>EX.NO: 4</b>	<b>DESIGN AND IMPLEMENTATION OF MAGNITUDE COMPARATOR</b>
<b>DATE :</b>	

**AIM:**

To design and implement

- (i) 2-bit magnitude comparator using logic gates.
- (ii) 8-bit magnitude comparator using IC 7485.

**APPARATUS REQUIRED:**

SL.NO	COMPONENT	SPECIFICATION	QUANTITY
1.	IC Trainer kit	-	
2.	EX-OR gate	IC7486	1
3.	NOT gate	IC7404	1
4.	OR gate	IC7432	1
5.	AND gate	IC7408	1
6.	4-bit Magnitude Comparator	IC 7485	2
7.	Connecting Wires	-	Few

**THEORY:**

A *magnitude comparator* is a combinational circuit that compares two given numbers (A and B) and determines whether one is equal to, less than or greater than the other. The output is in the form of three binary variables representing the conditions  $A = B$ ,  $A > B$  and  $A < B$ , if A and B are the two numbers being compared.

The two binary numbers A and B with two digits each, written in descending order as,

$$A = A_1A_0$$

$$B = B_1B_0$$

Each subscripted letter represents one of the digits in the number. It is observed from the bit contents of two numbers that  $A = B$ , when  $A_1 = B_1$  and  $A_0 = B_0$ . When the numbers are binary they possess the value of either 1 or 0, the equality relation of each pair can be expressed logically by the equivalence function as,




**HOD / ECE**



**LOGIC DIAGRAM:**

**2-bit Magnitude Comparator:**

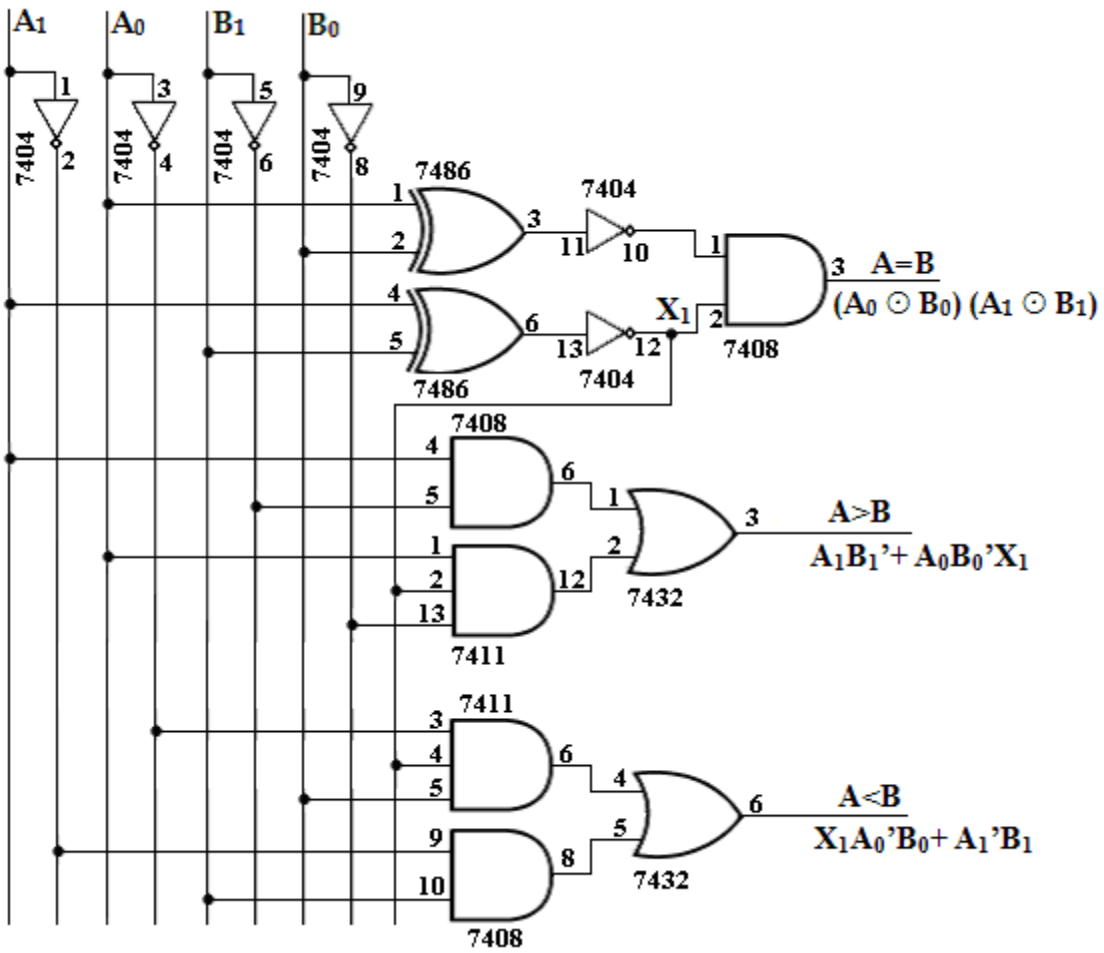

*Handwritten signature*

$$X_i = A_i B_i + A_i' B_i' \quad \text{for } i = 1, 2, 3, 4.$$

Or,  $X_i = (A \oplus B)'$  or,  $X_i' = A \oplus B$

Or,  $X_i = (A_i B_i' + A_i' B_i)'$

where,

$X_i = 1$  only if the pair of bits in position  $i$  are equal

To satisfy the equality condition of two numbers  $A$  and  $B$ , it is necessary that all  $X_i$  must be equal to logic 1. This indicates the AND operation of all  $X_i$  variables. In other words, we can write the Boolean expression for two equal 2-bit numbers.

$$(A = B) = X_1 X_0.$$

The binary variable  $(A=B)$  is equal to 1 only if all pairs of digits of the two numbers are equal.

To determine if  $A$  is greater than or less than  $B$ , we inspect the relative magnitudes of pairs of significant bits starting from the most significant bit. If the two digits of the most significant position are equal, the next significant pair of digits is compared. The comparison process is continued until a pair of unequal digits is found. It may be concluded that  $A > B$ , if the corresponding digit of  $A$  is 1 and  $B$  is 0. If the corresponding digit of  $A$  is 0 and  $B$  is 1, we conclude that  $A < B$ . Therefore, we can derive the logical expression of such sequential comparison by the following two Boolean functions,

$$(A > B) = A_1 B_1' + X_1 A_0 B_0'$$


$$(A < B) = A_1' B_1 + X_1 A_0' B_0$$

The symbols  $(A > B)$  and  $(A < B)$  are binary output variables that are equal to 1 when  $A > B$  or  $A < B$ , respectively.

### **8- BIT MAGNITUDE COMPARATOR:**



**HOD / ECE**

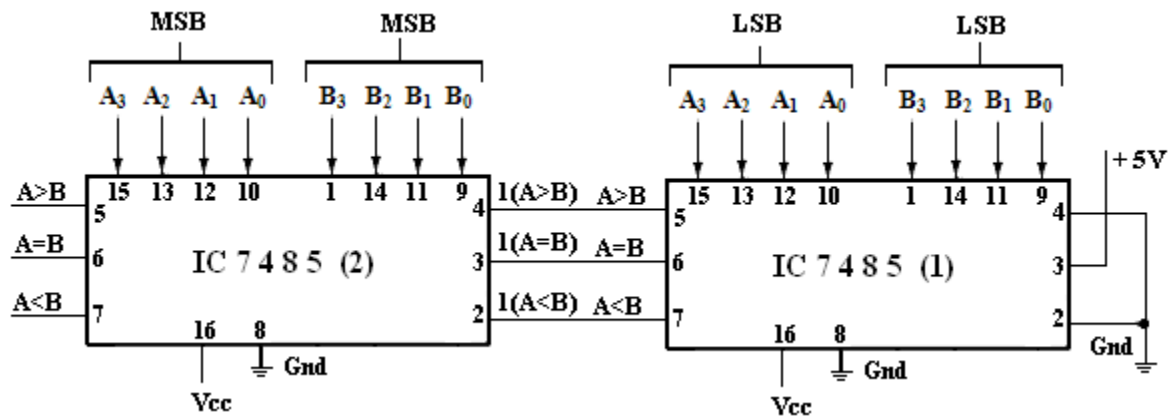

**Truth Table:**

A		B		A>B	A=B	A<B
0000	0000	0000	0000	0	1	0
0001	0001	0000	0000	1	0	0
0000	0000	0001	0001	0	0	1


**PROCEDURE:**

1. Connections are given as per the logic diagram.
2. Logic inputs are given as per the truth table.
3. Observe the logic output and verify with the truth tables.

**RESULT:**

Thus the 2-bit magnitude comparator was designed and implemented using logic gates and 8-bit magnitude comparator using IC 7485.

**4:1 MULTIPLEXER:**

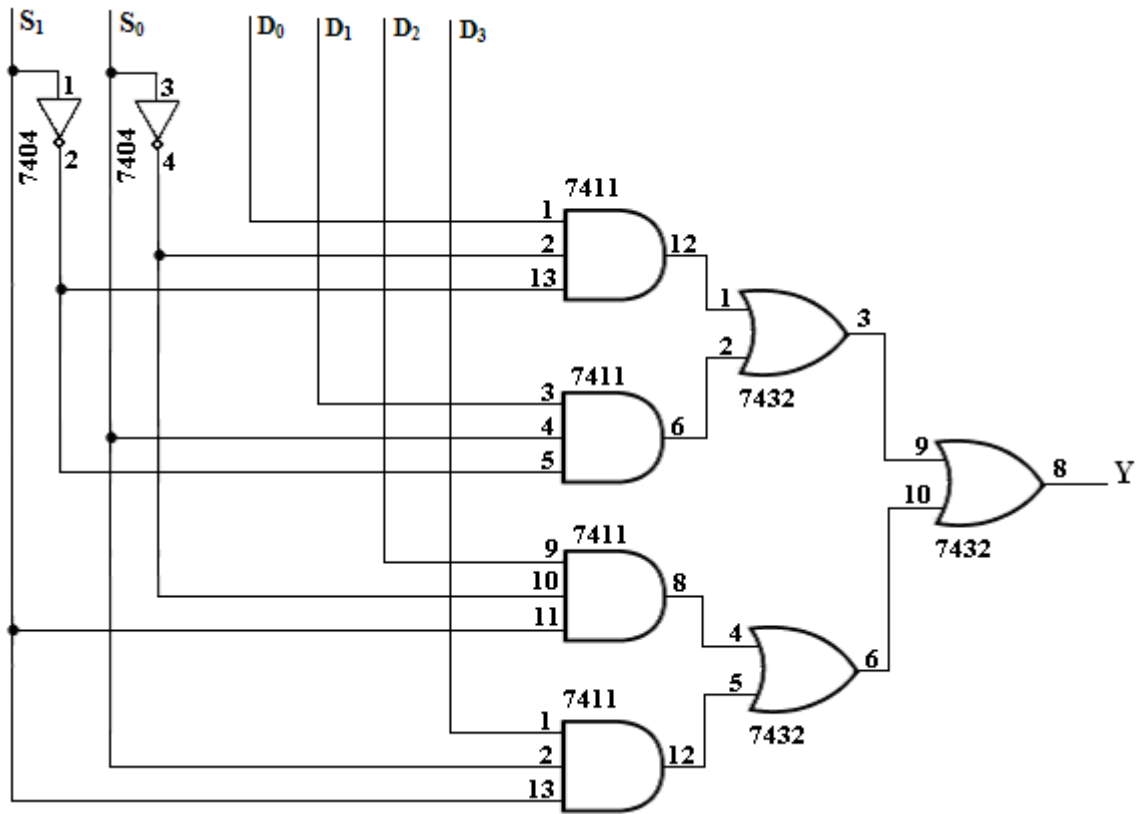

**Truth table:**

$S_1$	$S_0$	OUTPUTS, (Y)
0	0	$D_0$
0	1	$D_1$
1	0	$D_2$
1	1	$D_3$

*Handwritten signature*

**HOD / ECE**

**EX.NO: 5**

**DATE :**

**DESIGN AND IMPLEMENTATION OF  
MULTIPLEXER AND DEMULTIPLEXER**

**AIM:**

To design and implement multiplexer and demultiplexer using logic gates.

**APPARATUS REQUIRED:**

SL.NO	COMPONENT	SPECIFICATION	QUANTITY
1.	IC Trainer kit	-	1
2.	3-I/P AND GATE	IC7411	2
3.	NOT GATE	IC7404	1
4.	OR GATE	IC7432	1
5.	Patch cords	-	Few

**THEORY:**

**Multiplexer:**

Multiplexer means transmitting a large number of information units over a small number of channels or lines. A digital multiplexer is a combinational circuit that selects binary information from one of many input lines and directs it to a single output line. The selection of a particular input line is controlled by a set of selection lines. Normally there are  $2^n$  input line and 'n' selection lines whose bit combination determine which input is selected. It is called as **data selector**, because the output depends on the input data bit that is selected.

**Demultiplexer:**


The function of Demultiplexer is in contrast to multiplexer function. It takes information from one line and distributes it to a given number of output lines. For this reason, the demultiplexer is also known as a **data distributor**. Decoder can also be used as Demultiplexer.

In the 1:4 demultiplexer circuit, the data input line goes to all of the AND gates. The data select lines enable only one gate at a time and the data on the data input line will pass through the selected gate to the associated data output line.



**HOD / ECE**

**1: 4 DEMULTIPLEXER:**

 

**Truth Table:**

INPUT			OUTPUT			
$S_1$	$S_0$	I/P	$D_0$	$D_1$	$D_2$	$D_3$
0	0	0	0	0	0	0
0	0	1	1	0	0	0
0	1	0	0	0	0	0
0	1	1	0	1	0	0
1	0	0	0	0	0	0
1	0	1	0	0	1	0
1	1	0	0	0	0	0
1	1	1	0	0	0	1

*Handwritten signature*

**PROCEDURE:**

1. Connections are given as per the logic diagram.
2. Logic inputs are given as per the truth table.
3. Observe the logic output and verify with the truth tables.


**RESULT:**

Thus the multiplexer and demultiplexer was designed and implemented using logic gates.



**HOD / ECE**

 **Logic Diagram ( 2-to-4- Line Decoder with Enable Input):**



**Truth Table:**

INPUTS			OUTPUTS			
E	A	B	D <sub>0</sub>	D <sub>1</sub>	D <sub>2</sub>	D <sub>3</sub>
1	x	x	1	1	1	1
0	0	0	0	1	1	1
0	0	1	1	0	1	1
0	1	0	1	1	0	1
0	1	1	1	1	1	0

*Handwritten signature*



**EX.NO: 6**

**DATE :**

**DESIGN AND IMPLEMENTATION OF  
ENCODER AND DECODER**

**AIM:**

To design and implementation encoder and decoder using logic gates.

**APPARATUS REQUIRED:**

SL.NO	COMPONENT	SPECIFICATION	QUANTITY
1.	IC Trainer kit	-	1
2.	3-I/P NAND gate	IC7410	2
3.	NOT gate	IC7404	1
4.	OR gate	IC7432	3
5.	Patch cords	-	Few

**THEORY:**

**Encoder:**

An encoder is a digital circuit that performs inverse operation of a decoder. An encoder has  $2^n$  input lines and 'n' output lines. In encoder the output lines generates the binary code corresponding to the input value. In octal to binary encoder it has eight inputs, one for each octal digit and three output that generates the corresponding binary code. In encoder it is assumed that only one input has a value of one at any given time otherwise the circuit is meaningless. It has an ambiguity that when all inputs are zero the outputs are zero. The zero outputs can also be generated when  $D_0=1$ .


**Decoder:**

A decoder is a multiple output logic circuit which converts input into coded output where input and output codes are different. The input code generally has few bits than the output code. Each input code word produces a different output code word i.e., there is one to one mapping can be expressed in truth table. In block diagram of decoder circuit the encoded information is present as n input producing  $2^n$  possible outputs. The  $2^n$  output values are from 0 through out  $2^n-1$ .

**HOD / ECE**

**ENCODER:**

**Logic Diagram:**

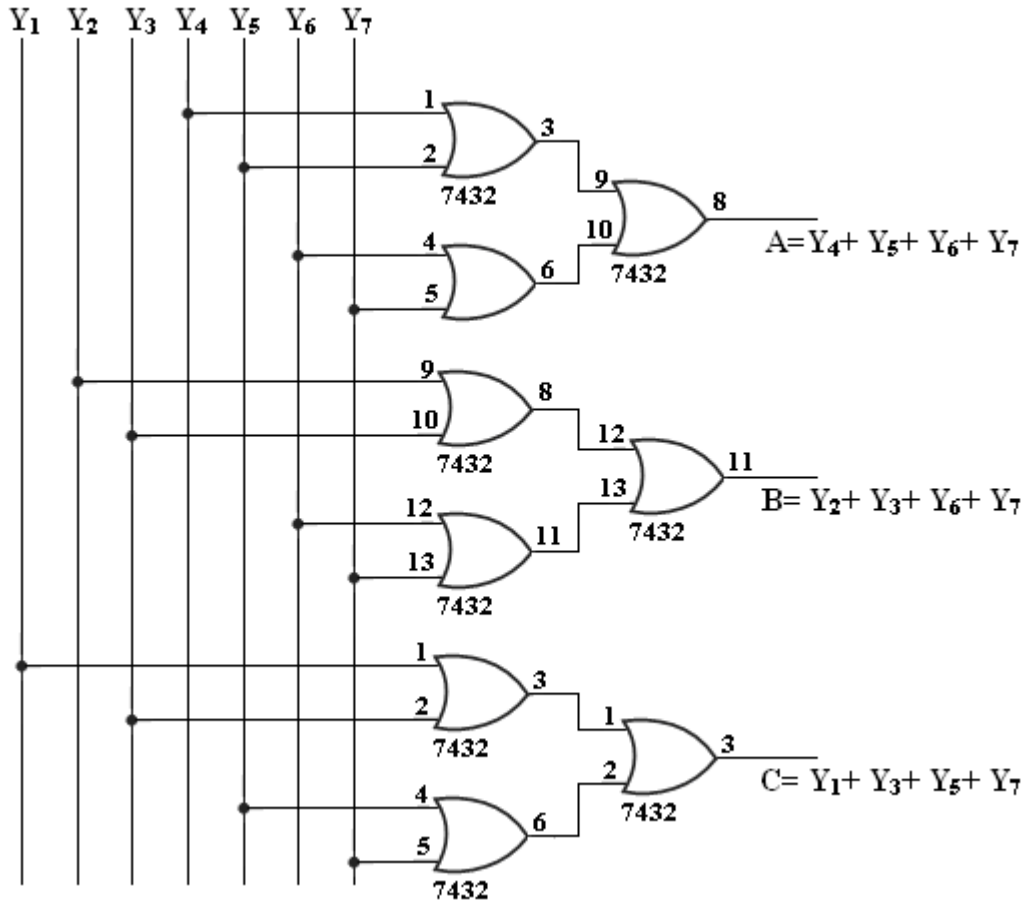

**Truth Table:**

INPUTS							OUTPUTS		
Y <sub>1</sub>	Y <sub>2</sub>	Y <sub>3</sub>	Y <sub>4</sub>	Y <sub>5</sub>	Y <sub>6</sub>	Y <sub>7</sub>	A	B	C
1	0	0	0	0	0	0	0	0	1
0	1	0	0	0	0	0	0	1	0
0	0	1	0	0	0	0	0	1	1
0	0	0	1	0	0	0	1	0	0
0	0	0	0	1	0	0	1	0	1
0	0	0	0	0	1	0	1	1	0
0	0	0	0	0	0	1	1	1	1

*Handwritten signature*

**PROCEDURE:**

1. Connections are given as per the logic diagram.
2. Logic inputs are given as per the truth table.
3. Observe the logic output and verify with the truth tables.

**RESULT:**


Thus the design and implementation of encoder and decoder using logic gates.



**HOD / ECE**

### 8- Bit ODD/EVEN PARITY GENERATOR/ CHECKER:

#### PIN DIAGRAM:

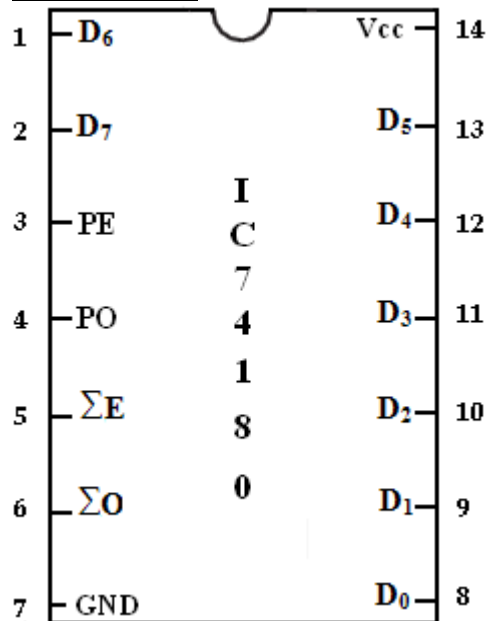


#### FUNCTION TABLE:

INPUTS			OUTPUTS	
	PE	PO	ΣE	ΣO
Number of Data Inputs (D <sub>0</sub> - D <sub>7</sub> )				
EVEN	1	0	1	0
ODD	1	0	0	1
EVEN	0	1	0	1
ODD	0	1	1	0
X	1	1	0	0
X	0	0	1	1

### 16- Bit ODD/EVEN PARITY GENERATOR:

#### LOGIC DIAGRAM:

*Handwritten signature*

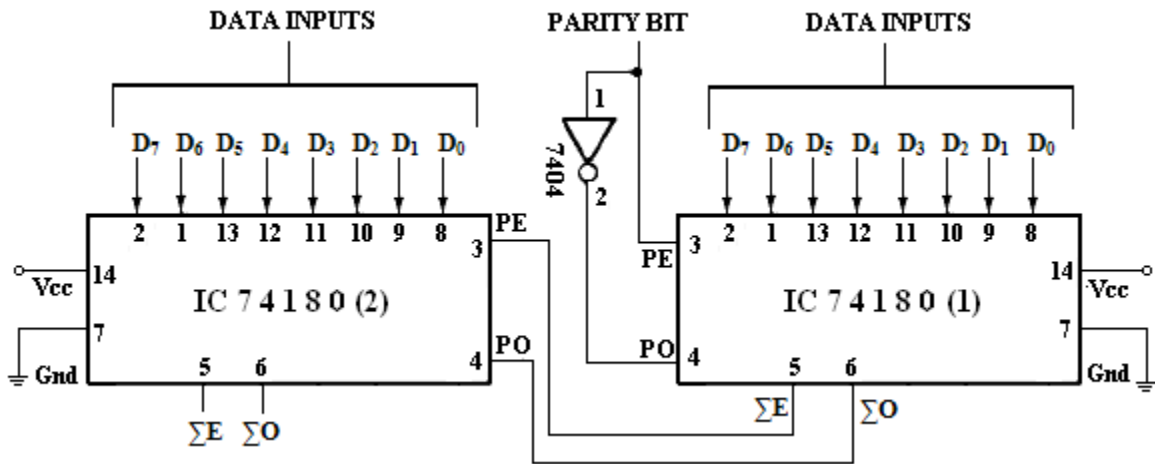

EX.NO: 7 DATE :	<b>DESIGN AND IMPLEMENTATION OF          16-BIT ODD/EVEN          PARITY GENERATOR/CHECKER</b>
--------------------	--

**AIM:**

To design and implement 16 bit odd /even parity checker generator using IC 74180.

**APPARATUS REQUIRED:**

SL.NO	COMPONENTS	SPECIFICATION	QUANTITY
1.	IC Trainer kit	-	1
2.	NOT gate	IC7404	1
3.	8-bit parity generator/ checker	IC74180	2
4.	Patch cords	-	Few

**THEORY:**

A *Parity* is a very useful tool in information processing in digital computers to indicate any presence of error in binary information. External noise and loss of signal strength causes loss of data bit information while transporting data from one device to other device, located inside the computer or externally. To indicate any occurrence of error, an extra bit is included with the message according to the total number of 1s in a set of data, which is called *parity*.

*[Signature]*

**HOD / ECE**

If the extra bit is considered 0 if the total number of 1s is even and 1 for odd quantities of 1s in a set of data, then it is called *even parity*. On the other hand, if the extra bit is 1 for even quantities of 1s and 0 for an odd number of 1s, then it is called *odd parity*.


The message including the parity is transmitted and then checked at the receiving end for errors. An error is detected if the checked parity does not correspond with the one transmitted. The circuit that generates the parity bit in the transmitter is called a parity generator and the circuit that checks the parity in the receiver is called a parity checker.

**TRUTH TABLE:**

D <sub>7</sub> D <sub>6</sub> D <sub>5</sub> D <sub>4</sub> D <sub>3</sub> D <sub>2</sub> D <sub>1</sub> D <sub>0</sub>	D <sub>7</sub> D <sub>6</sub> D <sub>5</sub> D <sub>4</sub> D <sub>3</sub> D <sub>2</sub> D <sub>1</sub> D <sub>0</sub>	PE	PO	ΣE	ΣO
1 1 0 0 0 0 0 0	1 1 0 0 0 0 0 0	1	0	1	0
0	0				
1 1 0 0 0 0 0 0	1 1 0 0 0 0 0 0	0	1	0	1
0	0				
1 1 0 0 0 0 0 0	0 1 0 0 0 0 0 0	0	1	1	0
0	0				

**16- Bit ODD/EVEN PARITY CHECKER:**

**LOGIC DIAGRAM:**

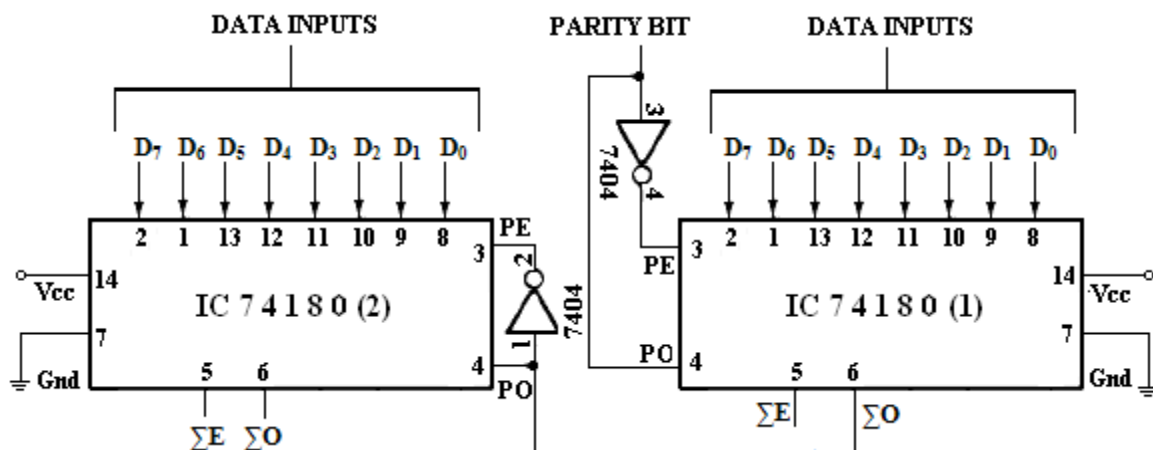

**TRUTH TABLE:**

*Handwritten signature*

<b>D<sub>7</sub> D<sub>6</sub> D<sub>5</sub> D<sub>4</sub> D<sub>3</sub> D<sub>2</sub> D<sub>1</sub> D<sub>0</sub></b>	<b>D<sub>7</sub>' D<sub>6</sub>' D<sub>5</sub>' D<sub>4</sub>' D<sub>3</sub>' D<sub>2</sub>' D<sub>1</sub>' D<sub>0</sub>'</b>	<b>PE</b>	<b>PO</b>	<b>ΣE</b>	<b>ΣO</b>
0 0 0 0 0 0 0 0 1	0 0 0 0 0 0 0 0	0	1	1	0
0 0 0 0 0 1 1 0	0 0 0 0 0 1 1 0	1	0	1	0
0 0 0 0 0 1 1 0	0 0 0 0 0 1 1 0	0	1	0	1

The parity checker circuit produces a check bit and is very similar to the parity generator circuit. If the check bit is 1, then it is assumed that the received data is incorrect. The check bit will be 0 if the received data is correct. The table shows the truth table for the even parity checker.

In even parity, the added parity bit will make the total number 1's even amount. In odd parity, the added parity bit will make the total number 1's odd amount. The parity checker circuit checks for possible errors in the transmission. If the information is passed in even parity, the bits required must have an even number of 1's. An error occur during transmission, if the received bits have an odd number of 1's indicating that one bit has changed in value during transmission.

**PROCEDURE:**

1. Connections are given as per the logic diagram.
2. Logic inputs are given as per the truth table.
3. Observe the logic output and verify with the truth tables




**HOD / ECE**

**RESULT:**

Thus the 16 bit odd /even parity checker generator was designed and implemented using IC 74180.

**4- BIT RIPPLE COUNTER:**

**PIN DIAGRAM: (JK Flip-Flop)**

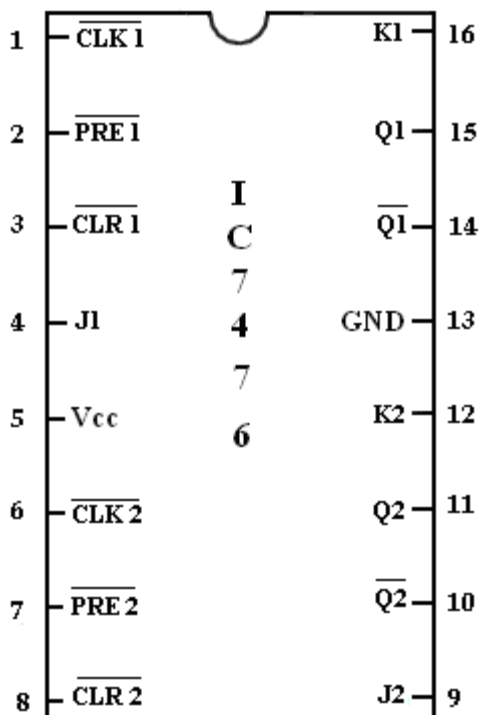

**Function Table for 7476:**

**HOD / ECE**



Inputs					Outputs	
Preset	Clear	Clock	J	K	Q	Q'
0	1	X	X	X	1	0
1	0	X	X	X	0	1
0	0	X	X	X	1	1
1	1	↓	0	0	No Change	
1	1	↓	0	1	0	1
1	1	↓	1	0	1	0
1	1	↓	1	1	Toggle	

<b>EX.NO: 8</b>  <b>DATE :</b>	<b>CONSTRUCTION AND VERIFICATION OF 4-BIT RIPPLE COUNTER &amp; MOD-10/ MOD-12 RIPPLE COUNTERS</b>
--------------------------------------	---

**AIM:**

To construct and verify 4 bit ripple counter, MOD-10 and MOD-12 ripple counter.

**APPARATUS REQUIRED:**

SL.NO	COMPONENTS	SPECIFICATION	QUANTITY
1.	IC Trainer kit	-	1
2.	JK Flip-flop	IC7476	2
3.	NAND gate	IC7400	1
4.	Patch cords	-	Few

**THEORY:**

A counter is a register capable of counting number of clock pulse arriving at its clock input. Counter represents the number of clock pulse arrived. A specified

*Handwritten signature*


**HOD / ECE**

sequence of states appears as counter output. This is the main difference between a register and a counter. There are two types of counter, synchronous and asynchronous. In synchronous common clock is given to all flip flop and in asynchronous, first flip flop is clocked by external pulse and then each successive flip flop is clocked by Q or Q' output of pervious stage.

A **ripple counter** is a cascaded arrangement of flip-flops where the output of one flip-flop drives the clock input of the following flip-flop. The number of flip-flops in the cascaded arrangement depends upon the number of different logic states that it goes through before it repeats the sequence, a parameter known as the modulus of the counter.

In a ripple counter, also called an *asynchronous counter* or a *serial counter*, the clock input is applied only to the first flip-flop, also called the input flip-flop, in the cascaded arrangement. The clock input to any subsequent flip-flop comes from the output of its immediately preceding flip-flop. For instance, the output of the first flip-flop acts as the clock input to the second flip-flop, the output of the second flip-flop feeds the clock input of the third flip-flop and so on.

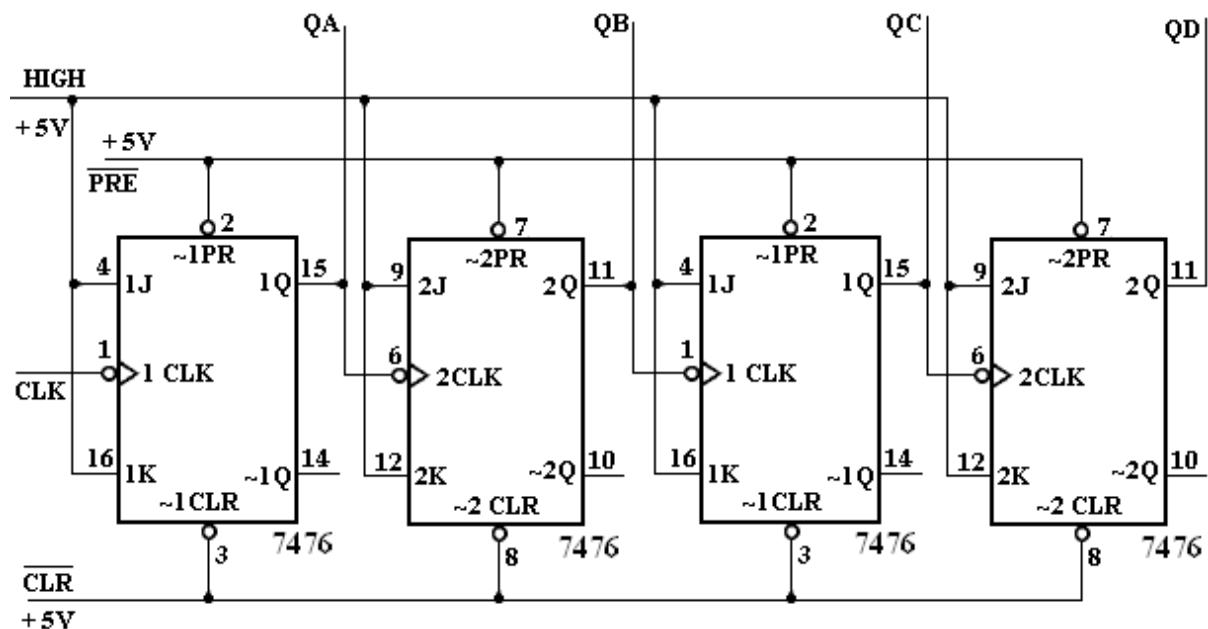**LOGIC DIAGRAM: (4-Bit Ripple Counter)**



**TRUTH TABLE:**

CLK	QA	QB	QC	QD
0	0	0	0	0

*Handwritten signature*


1	1	0	0	0
2	0	1	0	0
3	1	1	0	0
4	0	0	1	0
5	1	0	1	0
6	0	1	1	0
7	1	1	1	0
8	0	0	0	1
9	1	0	0	1
10	0	1	0	1
11	1	1	0	1
12	0	0	1	1
13	1	0	1	1
14	0	1	1	1
15	1	1	1	1

A four-bit ripple counter is implemented with negative edge-triggered *J-K* flip-flops wired as toggle flip-flops. The output of the first flip-flop feeds the clock input of the second, and the output of the second flip-flop feeds the clock input of the third, the output of which in turn feeds the clock input of the fourth flip-flop. The outputs of the four flip-flops are designated as Q0 (LSB flip-flop), Q1, Q2 and Q3 (MSB flip-flop).

**LOGIC DIAGRAM: (MOD-10 Ripple Counter)**



**HOD / ECE**

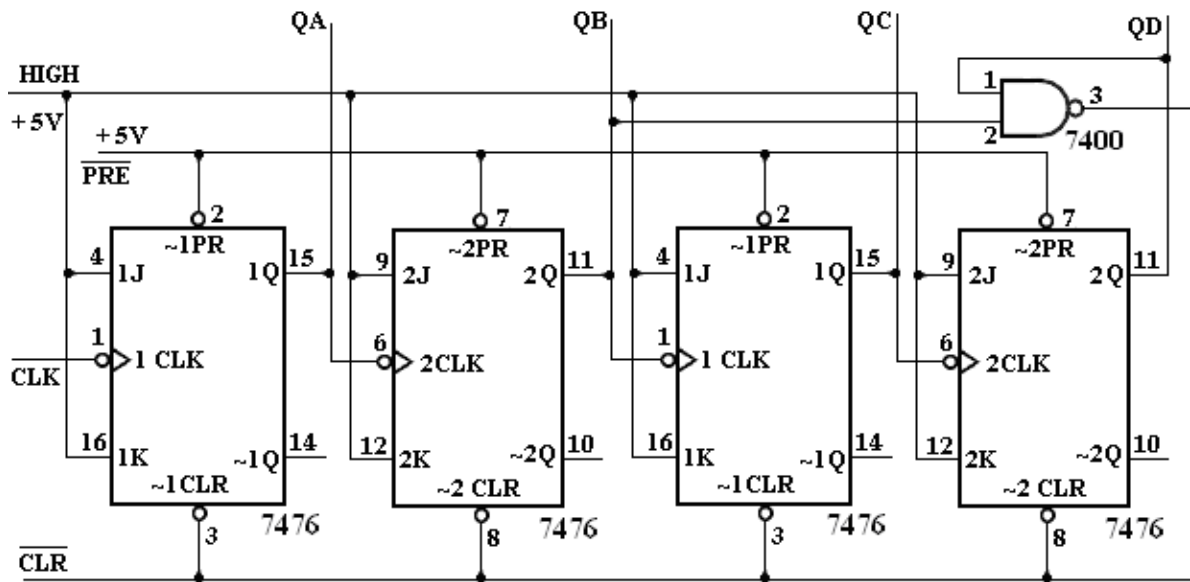


**TRUTH TABLE:**

CLK	QA	QB	QC	QD
0	0	0	0	0
1	1	0	0	0
2	0	1	0	0
3	1	1	0	0
4	0	0	1	0
5	1	0	1	0
6	0	1	1	0
7	1	1	1	0
8	0	0	0	1
9	1	0	0	1
10	0	0	0	0

**LOGIC DIAGRAM: (MOD-12 Ripple Counter)**

*Handwritten signature*

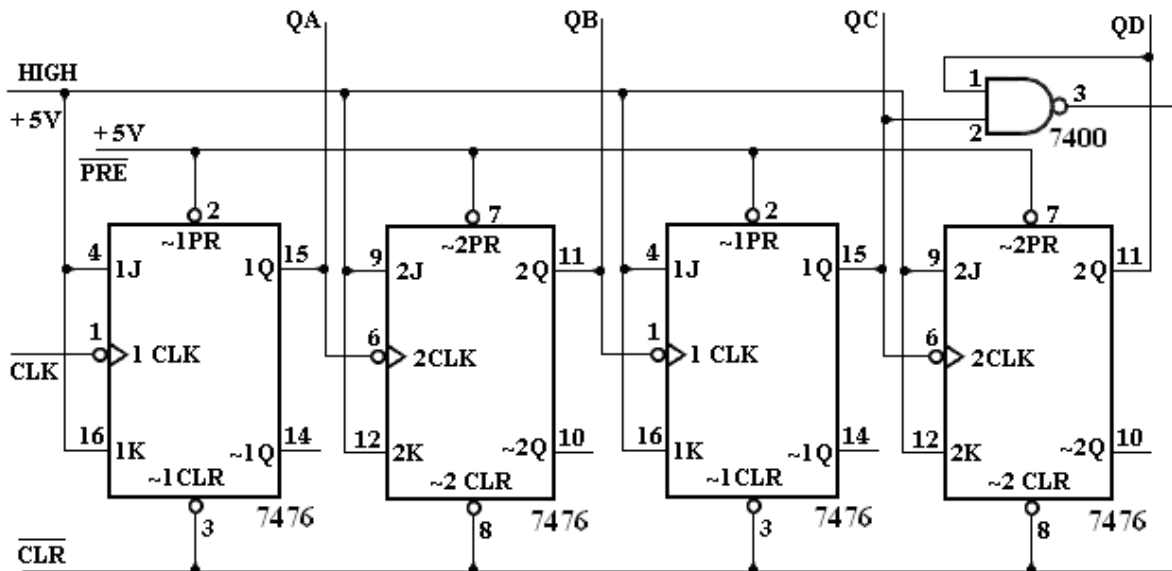

**TRUTH TABLE:**

CLK	QA	QB	QC	QD
0	0	0	0	0
1	1	0	0	0
2	0	1	0	0
3	1	1	0	0
4	0	0	1	0
5	1	0	1	0
6	0	1	1	0
7	1	1	1	0
8	0	0	0	1
9	1	0	0	1
10	0	1	0	1
11	1	1	0	1
12	0	0	0	0

**PROCEDURE:**


1. Connections are given as per the logic diagram.
2. Logic inputs are given as per the logic diagram.
3. Observe the logic output and verify with the truth tables.

**RESULT:** Thus 4-bit ripple counter, MOD-10 and MOD-12 ripple counter was constructed and verified successfully.

**3- BIT SYNCHRONOUS UP/DOWN COUNTER:**

*Handwritten signature*

**STATE DIAGRAM:**

 

**TRUTH TABLE:**

Input Up/Down'	Present State			Next State			A		B		C	
	Q <sub>A</sub>	Q <sub>B</sub>	Q <sub>C</sub>	Q <sub>A+1</sub>	Q <sub>B+1</sub>	Q <sub>C+1</sub>	J <sub>A</sub>	K <sub>A</sub>	J <sub>B</sub>	K <sub>B</sub>	J <sub>C</sub>	K <sub>C</sub>
0	0	0	0	1	1	1	1	x	1	x	1	x
0	1	1	1	1	1	0	x	0	x	0	x	1
0	1	1	0	1	0	1	x	0	x	1	1	x
0	1	0	1	1	0	0	x	0	0	x	x	1
0	1	0	0	0	1	1	x	1	1	x	1	x
0	0	1	1	0	1	0	0	x	x	0	x	1
0	0	1	0	0	0	1	0	x	x	1	1	x
0	0	0	1	0	0	0	0	x	0	x	x	1
1	0	0	0	0	0	1	0	x	0	x	1	x
1	0	0	1	0	1	0	0	x	1	x	x	1
1	0	1	0	0	1	1	0	x	x	0	1	x
1	0	1	1	1	0	0	1	x	x	1	x	1
1	1	0	0	1	0	1	x	0	0	x	1	x
1	1	0	1	1	1	0	x	0	1	x	x	1
1	1	1	0	1	1	1	x	0	x	0	1	x
1	1	1	1	0	0	0	x	1	x	1	x	1

*Handwritten signature*

<b>EX.NO:</b> 9	<b>DESIGN AND IMPLEMENTATION OF 3-BIT SYNCHRONOUS UP/DOWN COUNTER</b>
<b>DATE :</b>	

**AIM:**

To design and implement 3 bit synchronous up/down counter using JK flip-flop.

**APPARATUS REQUIRED:**

SL.NO	COMPONENTS	SPECIFICATION	QUANTITY
1.	IC Trainer kit	-	1
2.	JK Flip-flop	IC7476	2
3.	3-I/P NAND gate	IC7411	1
4.	NOT gate	IC7404	1
5.	OR gate	IC7432	1
6.	EX-OR gate	IC7486	1
7.	Patch Cords		Few

**THEORY:**

A Counter is a register capable of counting number of clock pulse arriving at its clock input. Counter represents the number of clock pulses arrived. An up/down counter is one that is capable of progressing in increasing order or decreasing order through a certain sequence. An up/down counter is also called bi-directional counter. Usually up/down operation of the counter is controlled by up/down signal. When this signal high counter goes through up sequence and when up/down signal is low counter follows reverse sequence.

The counter counts upwards when UP control are logic '1' and DOWN control is logic '0'. In this case the clock input of each flip-flop other than the LSB flip-flop is fed from the normal output of the immediately preceding flip-flop. The counter counts downwards when the UP controls input are logic '0' and DOWN control is logic '1'. In this case, the clock input of each flip-flop other than the LSB flip-flop is fed from the complemented output of the immediately preceding flip-flop.



**HOD / ECE**

**EXCITATION TABLE: (JK Flip-Flop)**

Q	Q <sub>t+1</sub>	J	K
0	0	0	x
0	1	1	x
1	0	x	1
1	1	x	0

**K-MAP SIMPLIFICATION:**

**For J<sub>A</sub>**

UD QA \ QB QC	00	01	11	10
00	1	0	0	0
01	X	X	X	X
11	X	X	X	X
10	0	0	1	0

$J_A = \overline{UD} \overline{QB} \overline{QC} + UD \overline{QB} \overline{QC}$

**For J<sub>B</sub>**

UD QA \ QB QC	00	01	11	10
00	1	0	X	X
01	1	0	X	X
11	0	1	X	X
10	0	1	X	X

$J_B = \overline{UD} \oplus \overline{QC}$

**For K<sub>A</sub>**

UD QA \ QB QC	00	01	11	10
00	X	X	X	X
01	1	0	0	0
11	0	0	1	0
10	X	X	X	X

$K_A = \overline{UD} \overline{QB} \overline{QC} + UD \overline{QB} \overline{QC}$

**For K<sub>B</sub>**

UD QA \ QB QC	00	01	11	10
00	X	X	0	1
01	X	X	0	1
11	X	X	1	0
10	X	X	1	0

$K_B = \overline{UD} \oplus \overline{QC}$

**For J<sub>C</sub>**

UD QA \ QB QC	00	01	11	10
00	1	X	X	1
01	1	X	X	1
11	1	X	X	1
10	1	X	X	1

$J_C = 1$

**For K<sub>C</sub>**


UD QA \ QB QC	00	01	11	10
00	X	1	1	X
01	X	1	1	X
11	X	1	1	X
10	X	1	1	X

$K_C = 1$

*Handwritten signature*



**LOGIC DIAGRAM:**

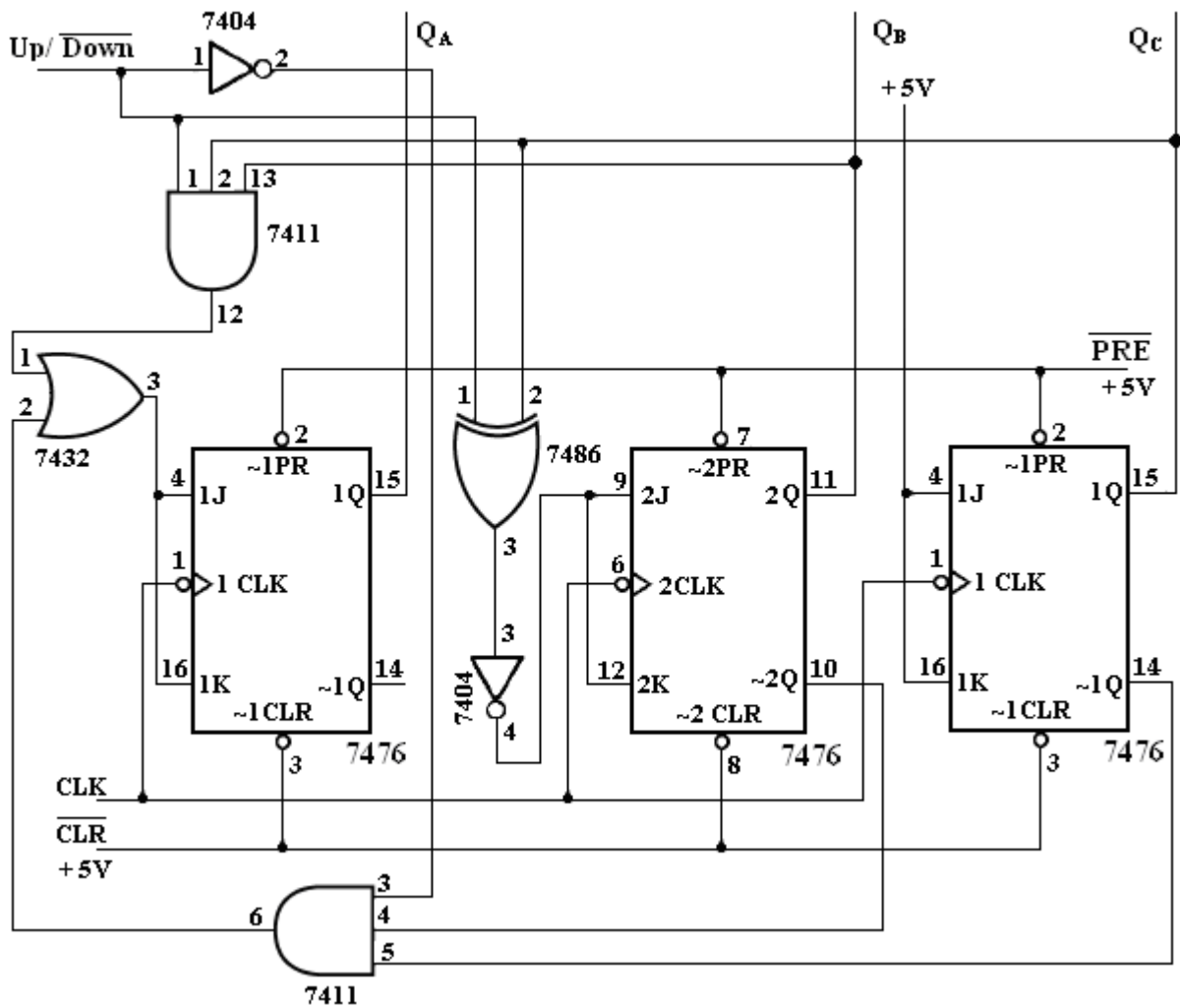

**PROCEDURE:**

1. Connections are given as per the logic diagram.
2. Logic inputs are given as per the logic diagram.
3. Observe the logic output and verify with the truth tables.


**RESULT:**

Thus 3- bit synchronous up/down counter was designed and implemented successfully.

**HOD / ECE**

**SHIFT REGISTER:**


**PIN DIAGRAM: (D-Flip-Flop)**

 

**Function Table:**

Inputs				Outputs	
Preset	Clear	Clock	D	Q	Q'
0	1	X	X	1	0
1	0	X	X	0	1
0	0	X	X	1	1
1	1	↑	0	0	1
1	1	↑	1	1	0
1	1	0	X	No Change	

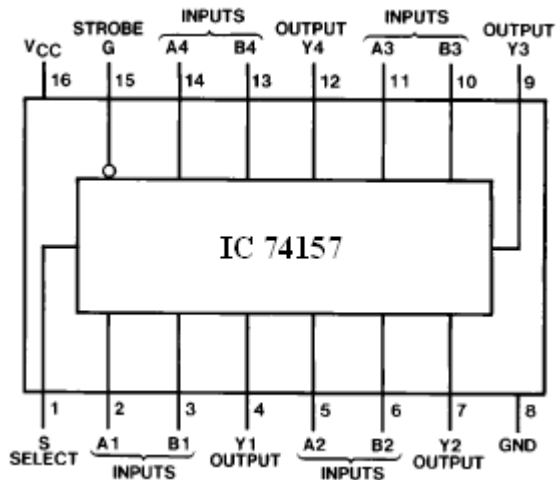**PIN DIAGRAM: (QUAD 2-LINE TO 1-LINE MULTIPLEXERS)**



*Handwritten signature*

<b>EX.NO:</b> 10	<b>IMPLEMENTATION OF SHIFT REGISTERS USING FLIP-FLOPS</b>
<b>DATE :</b>	

**AIM:**

To design and implement

1. Serial in serial Out(SISO)
2. Serial in parallel Out(SIPO)
3. Parallel in serial Out(PISO)
4. Parallel in parallel Out(PIPO)

**APPARATUS REQUIRED:**

SL.NO	COMPONENTS	SPECIFICATION	QUANTITY
1.	IC Trainer kit	-	1
2.	D-Flip flop	IC7474	2
3.	Quad 2-Line to 1-Line Multiplexer	IC74157	1
4.	Patch cords	-	Few

**THEORY:**

A register is capable of shifting its binary information in one or both directions is known as shift register. A logical configuration of shift register consist of a D flip flop cascaded with output of one flip flop connected to input of next flip flop. All flip flops receive common clock pulses which causes the shift in the output of the flip flop. The simplest possible shift register is one that uses only flip flop. The output of a given flip flop is connected to the input of next flip flop of the register. Each clock pulse shifts the content of register one bit position to right.




**HOD / ECE**

**Function Table: (74157)**

Inputs				Output Y
Strobe	Select	A	B	
H	X	X	X	L
L	L	L	X	L
L	L	H	X	H
L	H	X	L	L
L	H	X	H	H

**SERIAL IN SERIAL OUT:**

**LOGIC DIAGRAM:**

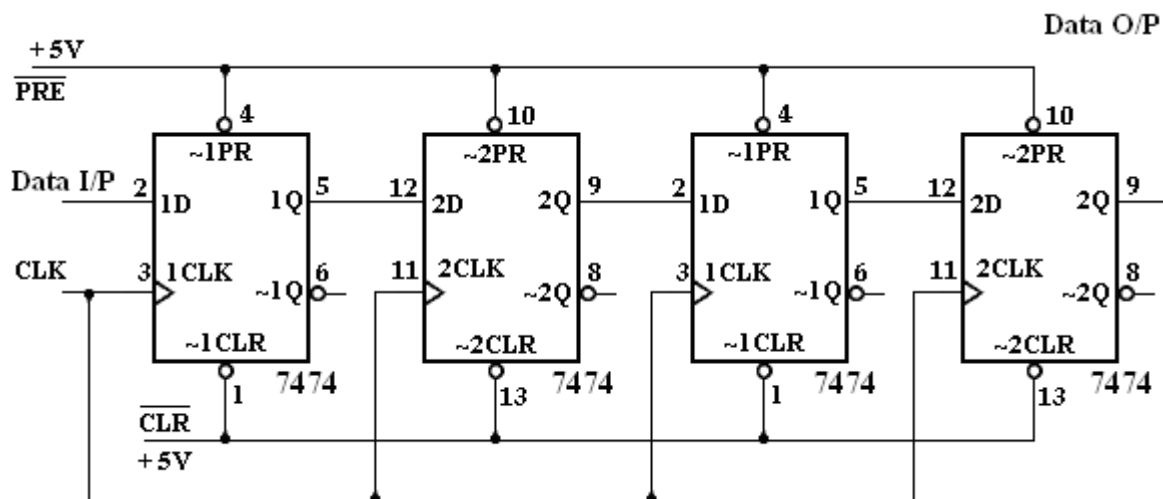


**TRUTH TABLE:**

CLK	Serial IN	Serial OUT
1	1	0
2	1	0
3	1	0
4	1	1
5	0	1
6	0	1
7	0	1
8	0	0

*Handwritten signature*

**Serial IN Parallel OUT:**

**LOGIC DIAGRAM:**

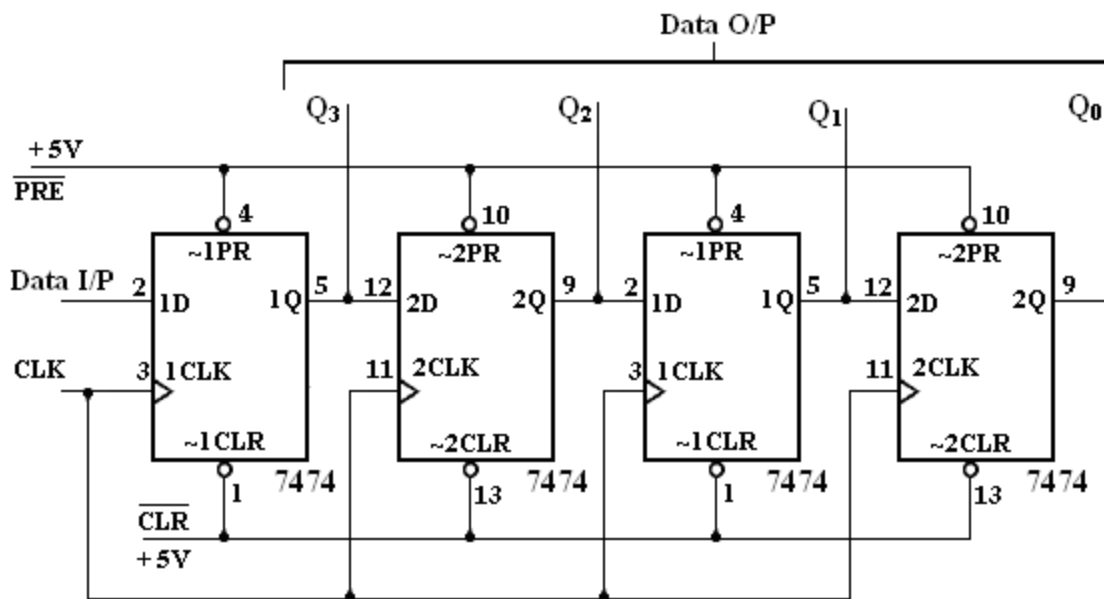


**TRUTH TABLE:**

CLK	DATA	OUTPUT			
		Q <sub>3</sub>	Q <sub>2</sub>	Q <sub>1</sub>	Q <sub>0</sub>
1	1	1	0	0	0
2	0	0	1	0	0
3	0	0	0	1	0
4	1	1	0	0	1

*Handwritten signature*

**Parallel IN Serial OUT:**

**LOGIC DIAGRAM:**

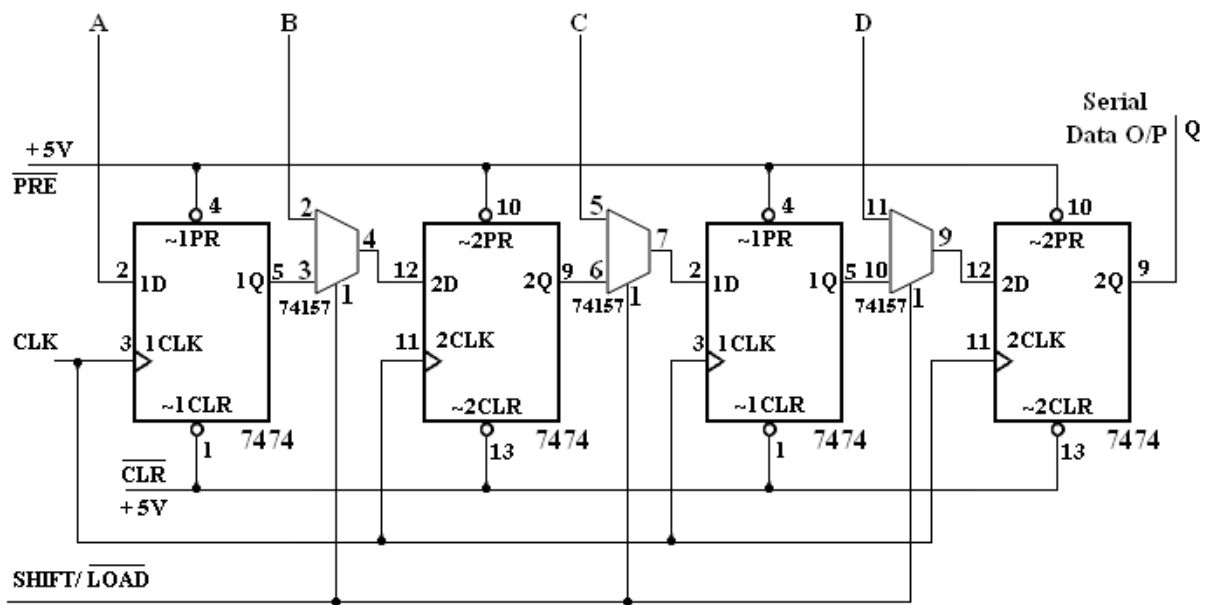

Note: Pin 15 (Strobe) of 74157 is connected to the ground


**TRUTH TABLE:**

SHIFT/ LOAD'	CLK	INPUTS				OUTPUT
		A	B	C	D	Q
0	0	1	0	1	0	0
1	1	1	0	1	0	1
1	2	1	0	1	0	0
1	3	1	0	1	0	1

*Handwritten signature*

**Parallel IN Parallel OUT:**

**Logic Diagram:**

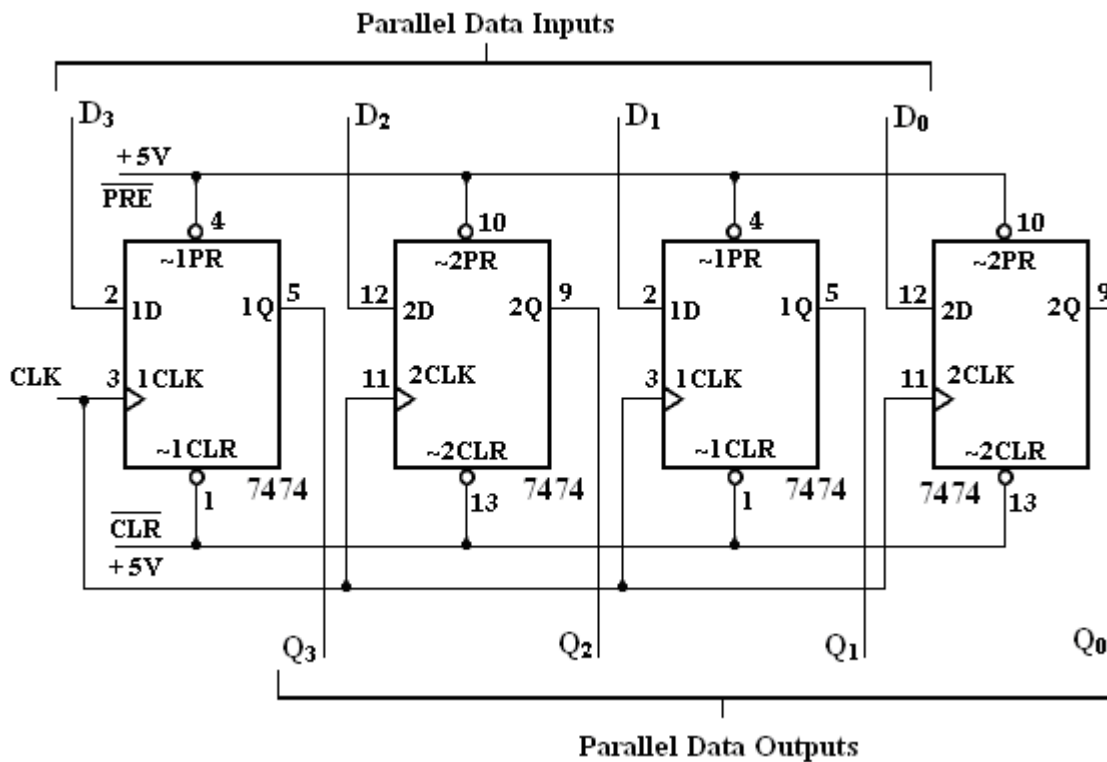

**TRUTH TABLE:**

CLK	DATA INPUTS				OUTPUT			
	D <sub>3</sub>	D <sub>2</sub>	D <sub>1</sub>	D <sub>0</sub>	Q <sub>3</sub>	Q <sub>2</sub>	Q <sub>1</sub>	Q <sub>0</sub>
1	1	0	0	1	1	0	0	1
2	1	0	1	0	1	0	1	0

**PROCEDURE:**

1. Connections are given as per the logic diagram.
2. Logic inputs are given as per the logic diagram.
3. Observe the logic output and verify with the truth tables.

**RESULT:**


Thus the design and implementation of

1. Serial in serial Out (SISO)
2. Serial in parallel Out (SIPO)
3. Parallel in serial Out (PISO)
4. Parallel in parallel Out (PIPO) were done successfully.

*Handwritten signature*

**Logic Diagram:**

**Fulladder using two half adders:**

 

**Truth Table:**

Inputs			Outputs	
x	y	C <sub>in</sub>	Sum (S)	Carry (C <sub>out</sub> )
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

*Handwritten signature*



<b>EX.NO: 11</b> <b>DATE :</b>	<b>VERILOG HARDWARE DESCRIPTION LANGUAGE</b>
-----------------------------------	--

**Aim:**

To design the following experiment using Verilog HDL

- Full adder and Full subtractor
- Multiplexer and Demultiplexer
- 4 – Bit Ripple Counter, MOD10 and MOD12 counter
- SISO, SIPO, PISO, PIPO Shift register

**Software Used:**

1. Xilinx 9.1i

**Program:**

**//Gate-level description of Full Adder using two Half Adder**

**//Description of Half Adder**

**module halfadder(s,co,x,y);**

**input x,y;**

**output s,co;**

**//Instantiate primitive gates**

**xor (s,x,y);**

**and (co,x,y);**

**endmodule**

**//Description of Full Adder**

**module fulladder(s,co,x,y,ci);**

**input x,y,ci;**

**output s,co;**

**wire s1,d1,d2; //Outputs of first XOR and AND gates**

**//Instantiate Half Adder**

**halfadder ha\_1(s1,d1,x,y);**

**halfadder ha\_2(s,d2,s1,ci);**

**or or\_gate(co,d2,d1);**


**endmodule**



**HOD / ECE**

**Logic Diagram:**

 **Full Subtractor using two half subtractors:**



**Truth table:**

Inputs			Outputs	
x	y	$B_{in}$	Difference(D)	Borrow( $B_{out}$ )
0	0	0	0	0
0	0	1	1	1
0	1	0	1	1
0	1	1	0	1
1	0	0	1	0
1	0	1	0	0
1	1	0	0	0
1	1	1	1	1

*Handwritten signature*

**Program:**

**//Gate-level description of Full Subtractor using two Half Subtractor**

**//Description of Half Subtractor**

**module** halfsubtractor(d,bo,x,y);

**input** x,y;

**output** d,bo;

**wire** z; **//Output of NOT gate**

**//Instatiate primitive gates**

**xor** (d,x,y);

**not** (z,x);

**and** (bo,z,y);

**endmodule**

**//Description of Full Subtractor**

**module** fullsubtractor(d,bo,x,y,bi);

**input** x,y,bi;

**output** d,bo;

**wire** a,g1,g2; **//Outputs of first XOR and AND gates**

**//Instantiate Half Subtractor**

halfsubtractor hs\_1(a,g1,x,y);

halfsubtractor hs\_2(d,g2,a,bi);


**or** or\_gate(bo,g2,g1);

**endmodule**



 **HOD / ECE**

**Logic Diagram:**  
**4 to 1 Multiplexer:**



**Truth table:**

INPUT		OUTPUT
s[1]	s[0]	y
0	0	D[0]
0	1	D[1]
1	0	D[2]
1	1	D[3]

*Handwritten signature*

**//Gate-level description of 4 to 1 Multiplexer**

```
module multiplexer(y,d,s);
```

```
output y;
```

```
input [3:0] d;
```

```
input [1:0] s;
```

```
wire a,b,c,e,f,g,h,i;
```

```
//Instantiate Primitive gates
```

```
not (a,s[1]);
```

```
not (b,s[0]);
```

```
and (c,d[0],b,a);
```

```
and (e,d[1],s[0],a);
```

```
and (f,d[2],b,s[1]);
```

```
and (g,d[3],s[0],s[1]);
```

```
or (h,c,e);
```


```
or (i,f,g);
```

```
or (y,h,i);
```

```
endmodule
```

**Logic Diagram:**

**1 to 4 Demultiplexer:**

 

*Handwritten signature*

**HOD / ECE**

**Truth Table:**

INPUT			OUTPUT			
s[1]	s[0]	D	y[0]	y[1]	y[2]	y[3]
0	0	0	0	0	0	0
0	0	1	1	0	0	0
0	1	0	0	0	0	0
0	1	1	0	1	0	0
1	0	0	0	0	0	0
1	0	1	0	0	1	0
1	1	0	0	0	0	0
1	1	1	0	0	0	1


**//Gate-level description of 1 to 4 Demultiplexer**

```

module demultiplexer(y,d,s);
output [3:0]y;
input d;
input [1:0] s;
wire a,b;
//Instantiate Primitive gates
not (a,s[1]);
not (b,s[0]);
and (y[0],d,b,a);
and (y[1],d,s[0],a);
and (y[2],d,b,s[1]);
and (y[3],d,s[0],s[1]);
endmodule

```

**LOGIC DIAGRAM: 4-Bit Ripple Counter:**

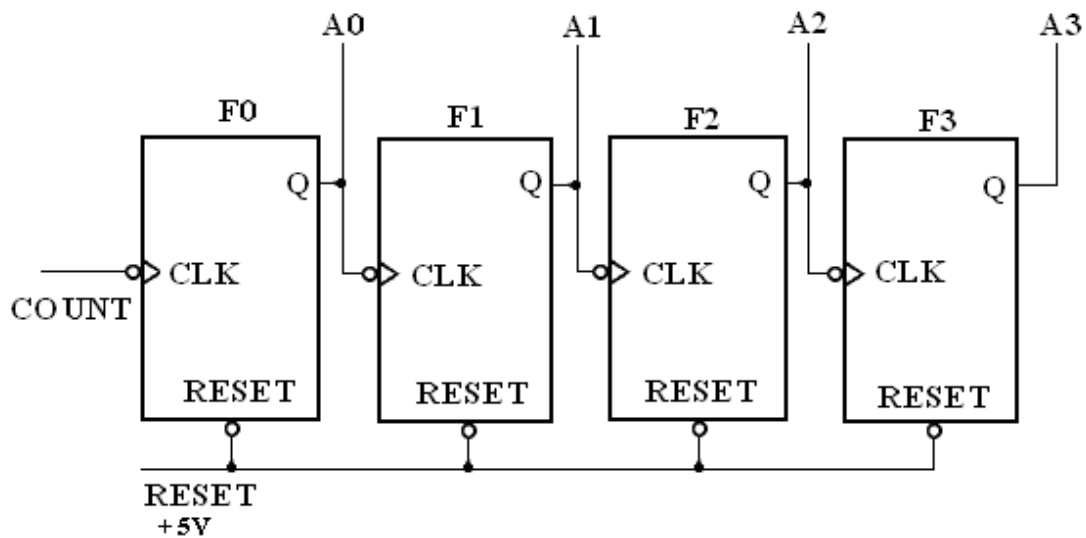

**TRUTH TABLE:**

*Handwritten signature*

COUNT	A0	A1	A2	A3
0	0	0	0	0
1	1	0	0	0
2	0	1	0	0
3	1	1	0	0
4	0	0	1	0
5	1	0	1	0
6	0	1	1	0
7	1	1	1	0
8	0	0	0	1
9	1	0	0	1
10	0	1	0	1
11	1	1	0	1
12	0	0	1	1
13	1	0	1	1
14	0	1	1	1
15	1	1	1	1

**//Structural description of Ripple Counter**

**module** ripplecounter(A0,A1,A2,A3,COUNT,RESET);

**output** A0,A1,A2,A3;

**input** COUNT,RESET;

**//Instantiate Flip-Flop**

FF F0(A0,COUNT,RESET);

FF F1(A1,A0,RESET);

FF F2(A2,A1,RESET);

FF F3(A3,A2,RESET);

**endmodule**

**//Description of Flip-Flop**

**module** FF(Q,CLK,RESET);

**output** Q;

**input** CLK,RESET;

**reg** Q;

**always** @(negedge CLK or negedge RESET)

**if**(~RESET)

Q=1'b0;

**else**


Q=(~Q);

**endmodule**

**LOGIC DIAGRAM:**



**MOD-10 Ripple Counter:**

 

**TRUTH TABLE:**

COUNT	A0	A1	A2	A3
0	0	0	0	0
1	1	0	0	0
2	0	1	0	0
3	1	1	0	0
4	0	0	1	0
5	1	0	1	0
6	0	1	1	0
7	1	1	1	0
8	0	0	0	1
9	1	0	0	1
10	0	0	0	0

//Structural description of MOD10 Counter

**HOD / ECE**




```
module MOD10(A0,A1,A2,A3,COUNT);  
output A0,A1,A2,A3;  
input COUNT;  
wire RESET;  
//Instantiate Flip-Flop  
FF F0(A0,COUNT,RESET);  
FF F1(A1,A0,RESET);  
FF F2(A2,A1,RESET);  
FF F3(A3,A2,RESET);  
//Instantiate Primitive gate  
nand (RESET,A1,A3);  
endmodule
```

```
//Description of Flip-Flop  
module FF(Q,CLK,RESET);  
output Q;  
input CLK,RESET;  
reg Q=1'b0;  
always @(negedge CLK or negedge RESET)  
if(~RESET)  
Q=1'b0;  
else  
Q=(~Q);  
endmodule
```



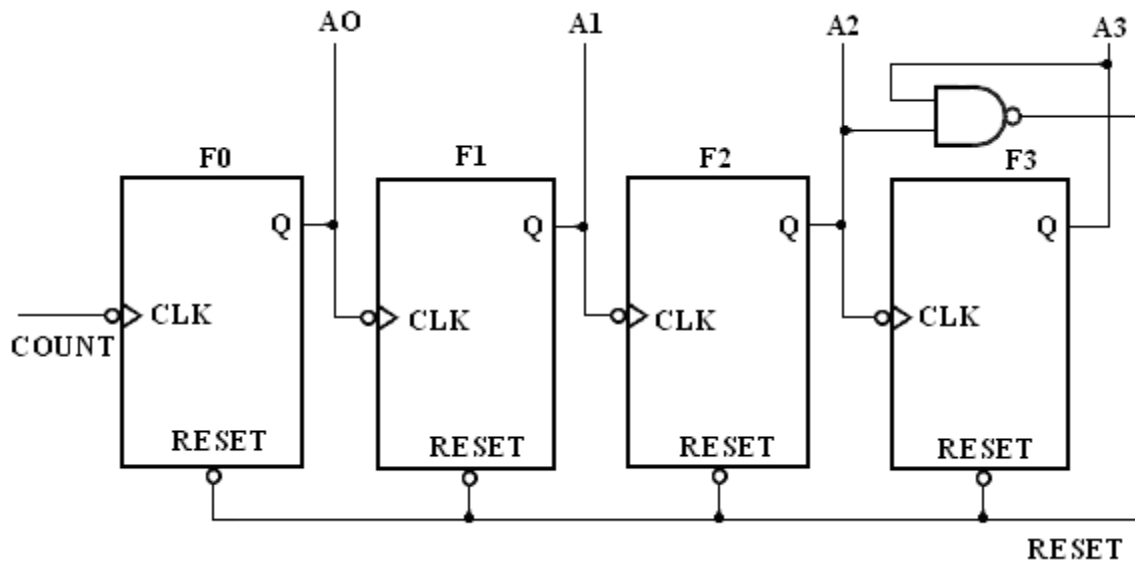**HOD / ECE**

**LOGIC DIAGRAM:**  
**MOD-12 Ripple Counter:**



**TRUTH TABLE:**

COUNT	A0	A1	A2	A3
0	0	0	0	0
1	1	0	0	0
2	0	1	0	0
3	1	1	0	0
4	0	0	1	0
5	1	0	1	0
6	0	1	1	0
7	1	1	1	0
8	0	0	0	1
9	1	0	0	1
10	0	1	0	1
11	1	1	0	1
12	0	0	0	0

*Handwritten signature*

**HOD / ECE**

```

//Structural description of MOD12 Counter
module MOD12(A0,A1,A2,A3,COUNT);
output A0,A1,A2,A3;
input COUNT;
wire RESET;
//Instantiate Flip-Flop
FF F0(A0,COUNT,RESET);
FF F1(A1,A0,RESET);
FF F2(A2,A1,RESET);
FF F3(A3,A2,RESET);
//Instantiate Primitive gates
nand (RESET,A2,A3);
endmodule


```

```

//Description of Flip-Flop
module FF(Q,CLK,RESET);
output Q;
input CLK,RESET;
reg Q=1'b0;
always @(negedge CLK or negedge RESET)
if(~RESET)
Q=1'b0;
else
Q=~Q;
endmodule

```

 **LOGIC DIAGRAM:**  
**SERIAL IN SERIAL OUT:**



**TRUTH TABLE:**

*Handwritten signature*

Clk	d	q
1	1	0
2	1	0
3	1	0
4	1	1
5	0	1
6	0	1
7	0	1
8	0	0

**//Structural description of Serial in Serial Out Shift Register**

**module** siso(q,d,clk);

**output** q;

**input** d,clk;

**wire** [2:0] a;

**dff** df1(a[0],d,clk);

**dff** df2(a[1],a[0],clk);

**dff** df3(a[2],a[1],clk);

**dff** df4(q,a[2],clk);

**endmodule**

**//Description of D - Flipflop**

**module** dff(q,d,clk);

**output** q;

**input** d,clk;

**reg** q=1'b0;

**always** @(posedge clk)

q=#5 d;


**endmodule**

**LOGIC DIAGRAM:**

**Serial IN Parallel OUT:**



**HOD / ECE**

 

**TRUTH TABLE:**

Clk	d	OUTPUT			
		Q[3]	Q[2]	Q[1]	Q[0]
1	1	1	0	0	0
2	1	1	1	0	0
3	1	1	1	1	0
4	1	1	1	1	1

**//Structural description of Serial in Parallel Out Shift Register**

```

module sipo(q,d,clk);
output [3:0] q;
input d,clk;
dff df1(q[3],d,clk);
dff df2(q[2],q[3],clk);
dff df3(q[1],q[2],clk);
dff df4(q[0],q[1],clk);
endmodule

```

**//Description of D - Flipflop**

```


module dff(q,d,clk);
output q;
input d,clk;
reg q=1'b0;
always @(posedge clk)
q=#5 d;
endmodule

```

**LOGIC DIAGRAM:**

**Parallel IN Serial OUT:**

*Handwritten signature*

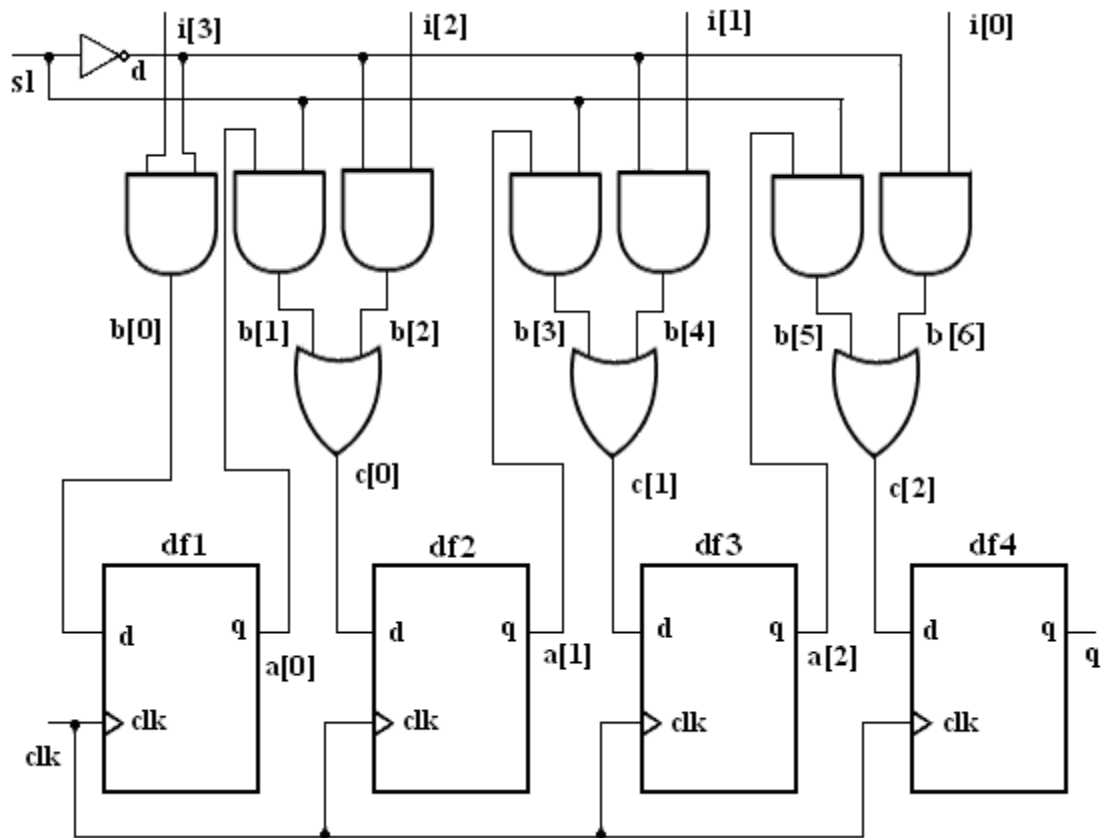

**TRUTH TABLE:**

Sl	Clk	INPUT				OUTPUT
		i[3]	i[2]	i[1]	i[0]	q
0	0	1	0	0	1	1
1	1	1	0	0	1	0
1	2	1	0	0	1	0
1	3	1	0	0	1	1

//Structural description of Parallel in Serial Out Shift Register

module piso(q,i,clk,sl);

*Handwritten signature*

HOD / ECE

```

output q;
wire [2:0] a;
wire [6:0] b;
wire [2:0] c;
wire d;
input clk,s1;
input [3:0]i;
//Instantiate D – Flipflop
dff df1(a[0],b[0],clk);
dff df2(a[1],c[0],clk);
dff df3(a[2],c[1],clk);
dff df4(q,c[2],clk);
//Instantiate Primitive gates
not (d,s1);
and (b[0],d,i[3]);
and (b[1],a[0],s1);
and (b[2],d,i[2]);
and (b[3],a[1],s1);
and (b[4],d,i[1]);
and (b[5],a[2],s1);
and (b[6],d,i[0]);
or (c[0],b[1],b[2]);
or (c[1],b[3],b[4]);
or (c[2],b[5],b[6]);
endmodule
//Description of D - Flipflop
module dff(q,d,clk);
output q;
input d,clk;
reg q=1'b0;
always @(posedge clk)
q=d;
endmodule


```

**Logic Diagram:**

**Parallel IN Parallel OUT:**



**HOD / ECE**

 

**TRUTH TABLE:**

Clk	INPUT				OUTPUT			
	d[3]	d[2]	d[1]	d[0]	q[3]	q[2]	q[1]	q[0]
1	1	0	1	0	1	0	1	0
2	1	0	0	1	1	0	0	1

**//Structural description of Parallel in Parallel Out Shift Register**

```

module pipo(q,d,clk);
output [3:0] q;
input [3:0] d;
input clk;
//Instantiate D - Flipflop
dff df1(q[3],d[3],clk);
dff df2(q[2],d[2],clk);
dff df3(q[1],d[1],clk);
dff df4(q[0],d[0],clk);
endmodule

```

**//Description of D - Flipflop**

```

module dff(q,d,clk);
output q;
input d,clk;
reg q=1'b0;
always @(posedge clk)
q=#5 d;
endmodule

```